

# First-Order High-Pass Butterworth Filter

①

High-pass filters are often formed simply by interchanging frequency-determining resistors and capacitors in low-pass filters. That is, a first order high-pass filter is formed from a first-order low pass filter by interchanging components  $R$  and  $C$ .

Figure 1 shows a first-order high-pass Butterworth filter with a low cutoff frequency of  $f_L$ . This is the frequency at which the magnitude of the gain is 0.707 times its passband value. Obviously, all frequencies higher than  $f_L$  are passband frequencies, with the highest frequency determined by the closed loop bandwidth of the op-amp.

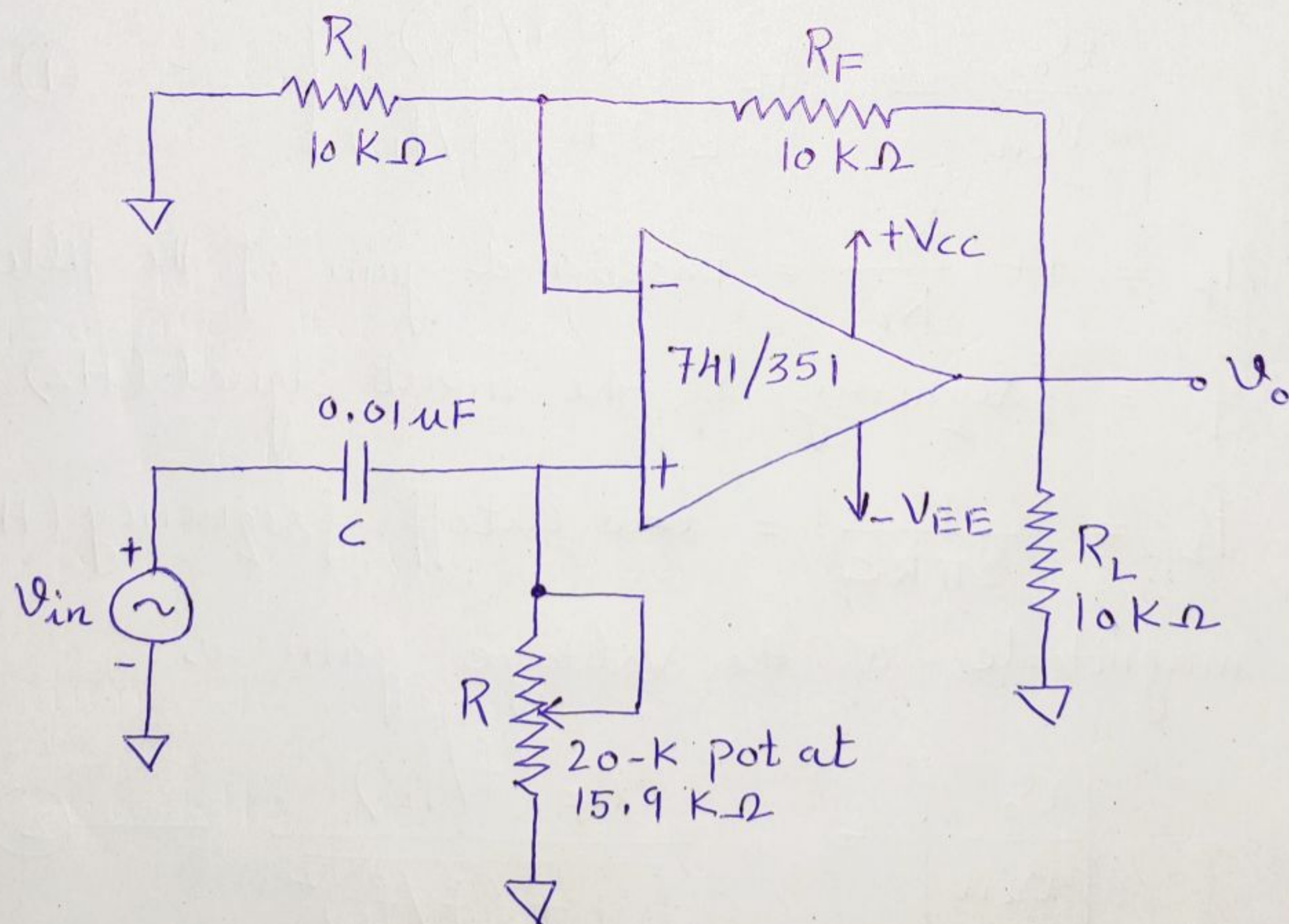


Figure 1. First-order high-pass Butterworth filter.



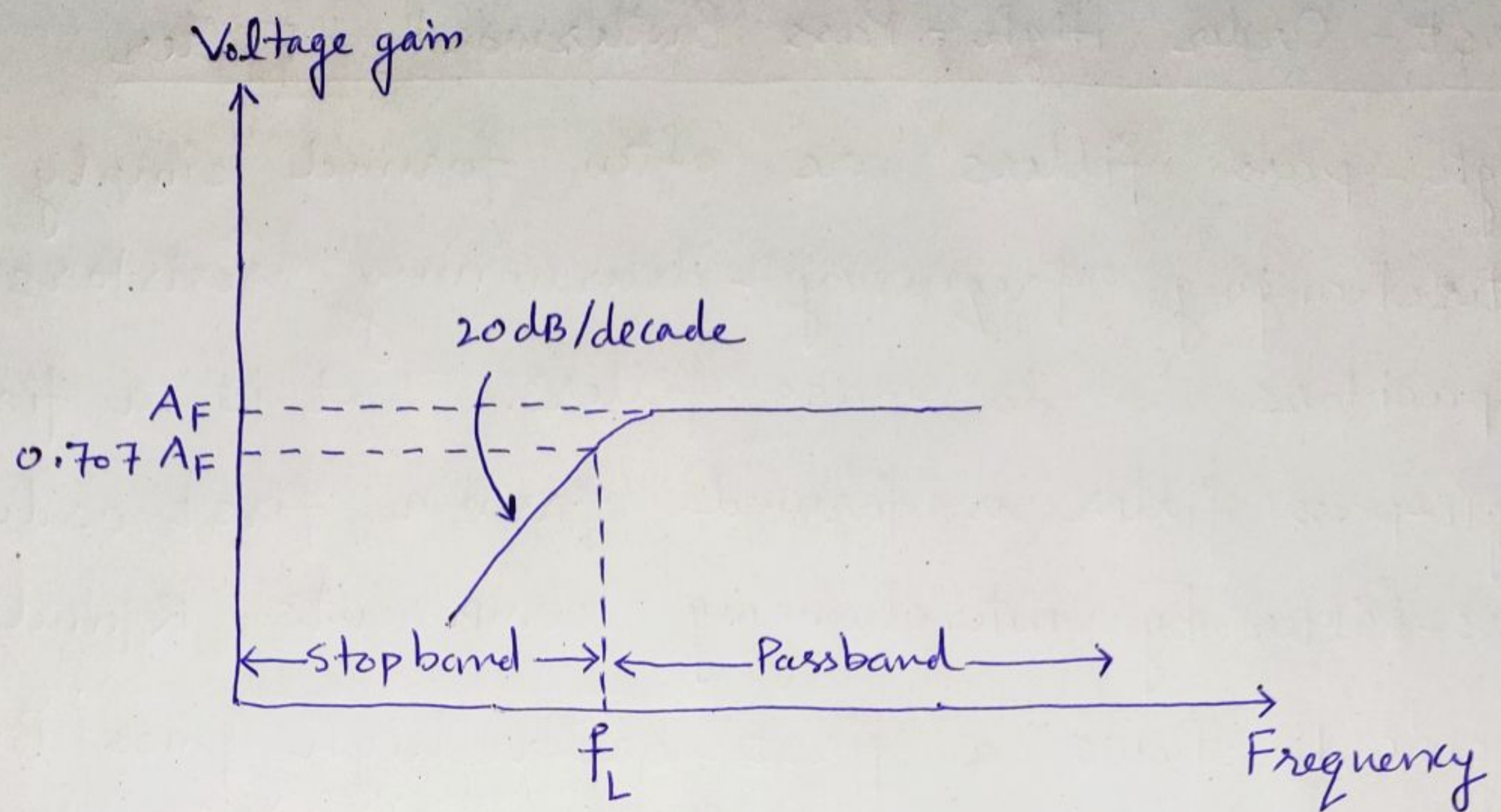


Figure 2. Frequency response of first-order high-pass Butterworth filter.

The first-order high-pass filter of Figure 1 has the output voltage given by,

$$V_o = \left(1 + \frac{R_F}{R_i}\right) \frac{j2\pi f RC}{1 + j2\pi f RC} V_{in}$$

or

$$\frac{V_o}{V_{in}} = A_F \left[ \frac{j(f/f_L)}{1 + j(f/f_L)} \right] \quad \text{--- (1)}$$

where  $A_F = 1 + \frac{R_F}{R_i}$  = passband gain of the filter

$f$  = frequency of the input signal (Hz)

$f_L = \frac{1}{2\pi RC}$  = low cutoff frequency (Hz)

Hence the magnitude of the voltage gain is

$$\left| \frac{V_o}{V_{in}} \right| = \frac{A_F (f/f_L)}{\sqrt{1 + (f/f_L)^2}} \quad \text{--- (2)}$$

Since high-pass filters are formed from low-pass filters simply by interchanging R's and C's, the design



and frequency scaling procedure of the low-pass filters<sup>(3)</sup> are also applicable to the high-pass filters.

Q1. Design a high-pass filter at a cutoff frequency of 1 KHz with a passband gain of 2.

Solution: Follow the design steps.

1.  $f_L = 1 \text{ KHz}$

2. Let  $C = 0.01 \mu\text{F}$

3. Then  $R = \frac{1}{2\pi f_L C} = \frac{1}{2\pi (10^3)(10^{-8})} = 15.9 \text{ K}\Omega$

4. Since the passband gain is 2,  $R_1$  and  $R_F$  must be equal. Therefore, let  $R_1 = R_F = 10 \text{ K}\Omega$ . The complete circuit is shown in Figure 1 along with the component values.

### Band Pass Filter

A band-pass filter has a passband between two cutoff frequencies  $f_H$  and  $f_L$  such that  $f_H > f_L$ . Any input frequency outside this passband is attenuated.

Basically, there are two types of band-pass filters: (1) wide band pass and (2) narrow bandpass. We will define a filter as wide band pass if its quality factor  $Q < 10$ . On the other hand, if  $Q > 10$ , we will call the filter a narrow band-pass filter. The relationship between  $Q$ , the 3-dB bandwidth



and the center frequency  $f_c$  is given by (4)

$$Q = \frac{f_c}{BW} = \frac{f_c}{f_H - f_L} \quad \text{--- (3)}$$

For the wide band-pass filter, the center frequency  $f_c$  can be defined as

$$f_c = \sqrt{f_H f_L} \quad \text{--- (4)}$$

where  $f_H$  = high cutoff frequency (Hz)

$f_L$  = low cutoff frequency of the wide band pass filter (Hz)

In a narrow band-pass filter, the output voltage peaks at the center frequency.

### Wide Band Pass Filter

A wide band-pass filter can be formed by simply cascading high-pass and low pass sections. The order of the band pass filter depends on the order of the high pass and low-pass filter section.

Figure 3 shows the  $\pm 20\text{dB/decade}$  wide band-pass filter, which is composed of first-order high pass and first-order low-pass filters. To realize a band-pass response,  $f_H$  must be larger than  $f_L$ .

The voltage gain magnitude of the band-pass filter is equal to the product of the voltage gain magnitudes of the high pass and low-pass filters.



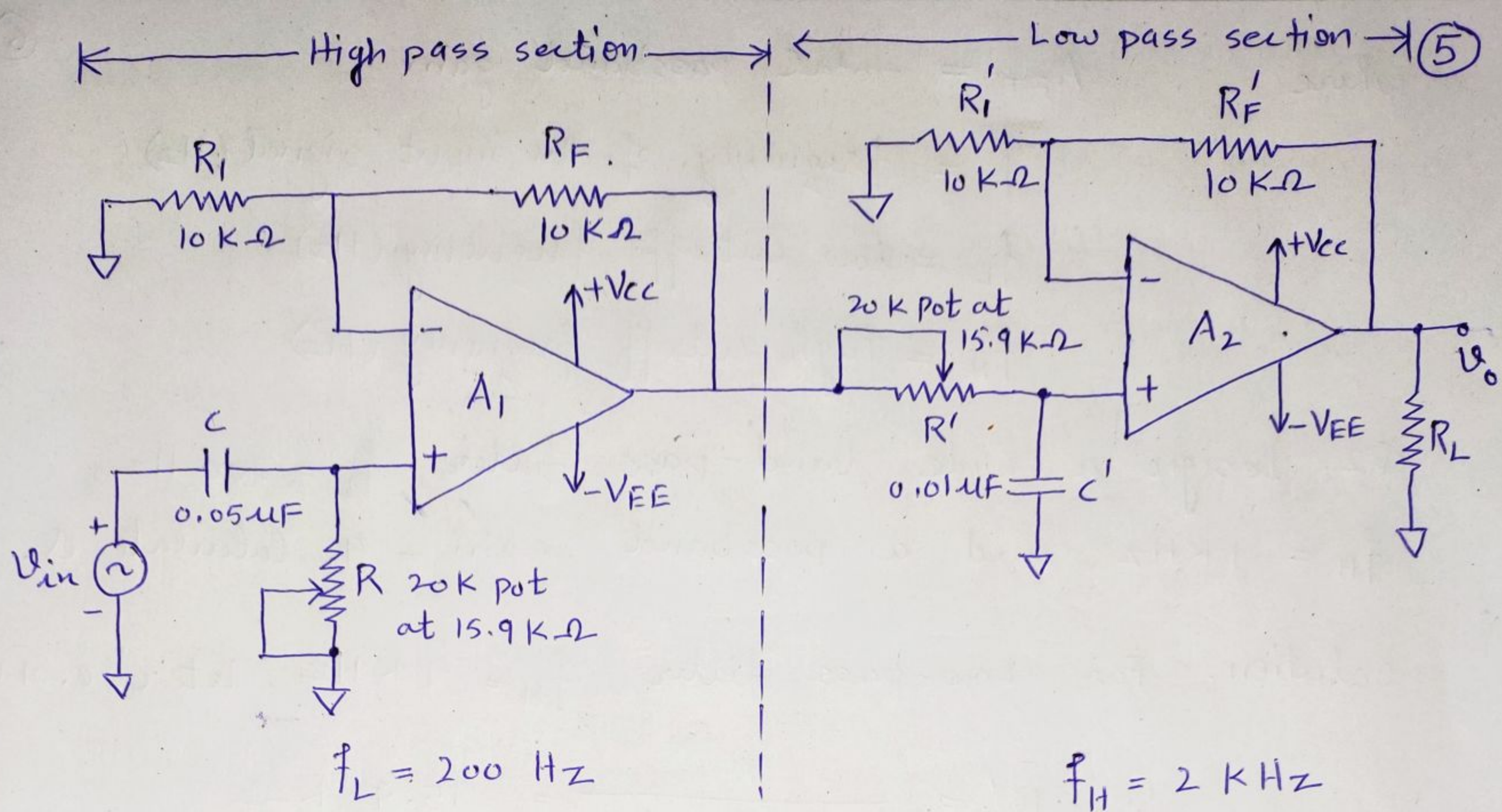


Figure 3.  $\pm 20 \text{ dB/decade}$  - wide band-pass filter.

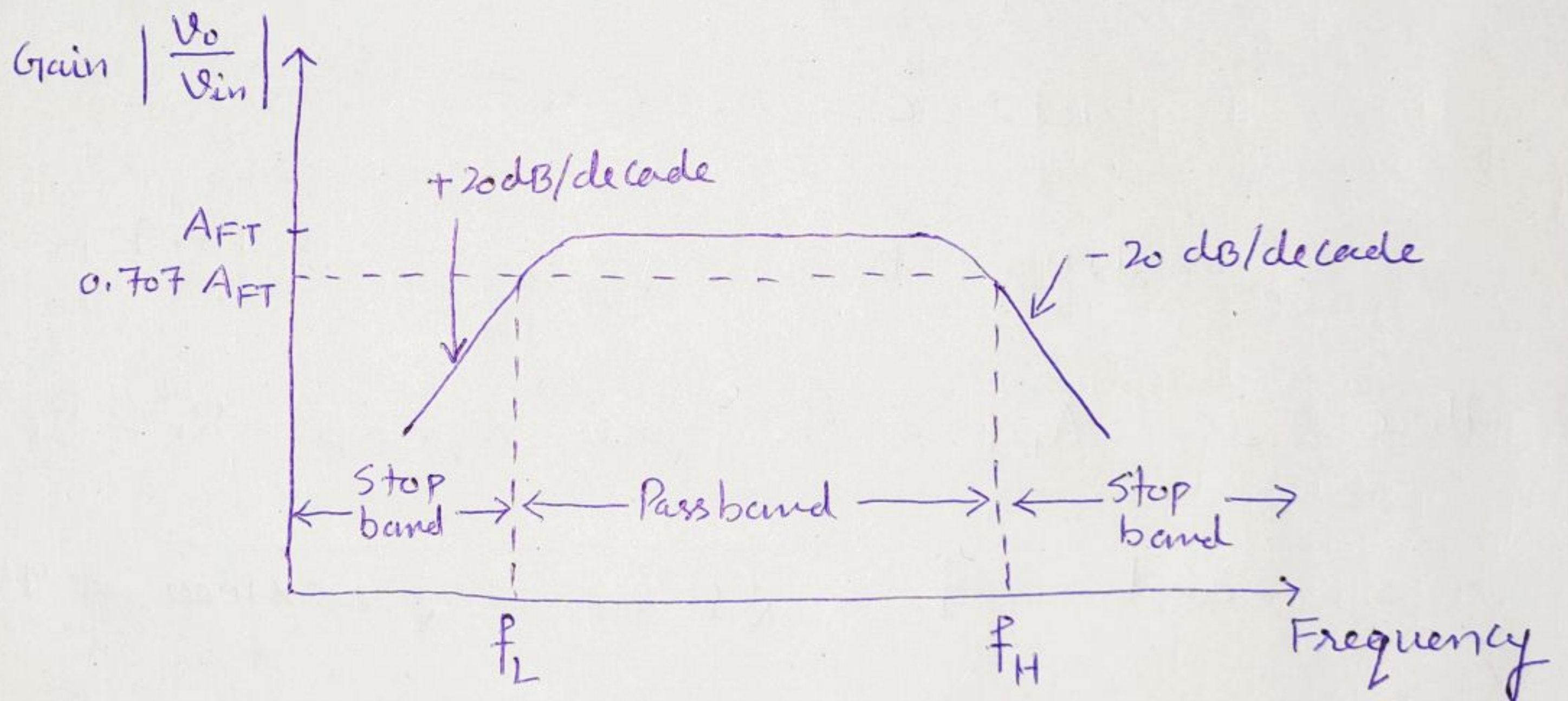


Figure 4. Frequency response of wide band-pass filter.

The frequency response of wide band-pass filter is shown in Figure 4. The gain (voltage) magnitude of wide band-pass filter is given by

$$\left| \frac{V_o}{V_{in}} \right| = \frac{A_{FT} (f/f_L)}{\sqrt{[1 + (f/f_L)^2][1 + (f/f_H)^2]}} \quad - (5)$$



where

$A_{FT}$  = total passband gain

$f$  = frequency of the input signal (Hz)

$f_L$  = low cutoff frequency (Hz)

$f_H$  = high cutoff frequency (Hz)

Q2. Design a wide band-pass filter  $f_L = 200$  Hz,  $f_H = 1$  KHz, and a passband gain = 4. Calculate Q.

Solution: For Low-pass filter,  $f_H = 1$  KHz, let  $C' = 0.01 \mu F$ .

$$\therefore R' = \frac{1}{2\pi f_H C'} = 15.9 \text{ K}\Omega$$

In the case of High-pass filter,  $f_L = 200$  Hz.

$$\text{let } C = 0.05 \mu F$$

$$\text{then } R = \frac{1}{2\pi f_L C} = 15.9 \text{ K}\Omega$$

Here

$$A_{FT} = 4 \text{ since } R_1 = R_F = R_1' = R_F' = 10 \text{ K}\Omega$$

$$\text{and } f_c = \sqrt{f_L f_H} = \sqrt{200 \times 1000} = 447.2 \text{ Hz}$$

$$\therefore Q = \frac{447.2}{1000 - 200} = 0.56 \text{ (Answer)}$$

---