

# Feedback Amplifiers

①

## Classification of Basic Amplifiers

The basic amplifiers are normally classified into four categories based on the magnitudes of the input and output impedances of an amplifier, with respect to the source and load impedances. These basic amplifiers are used in feedback amplifiers.

1. Voltage Amplifiers
2. Current Amplifiers
3. Transconductance Amplifier
4. Transresistance Amplifier

### 1. Voltage Amplifier

A voltage amplifier is represented by a two-port network. It is driven by a voltage source  $V_s$  with source resistance  $R_s$ . An external load resistance  $R_L$  is connected across the output terminals.

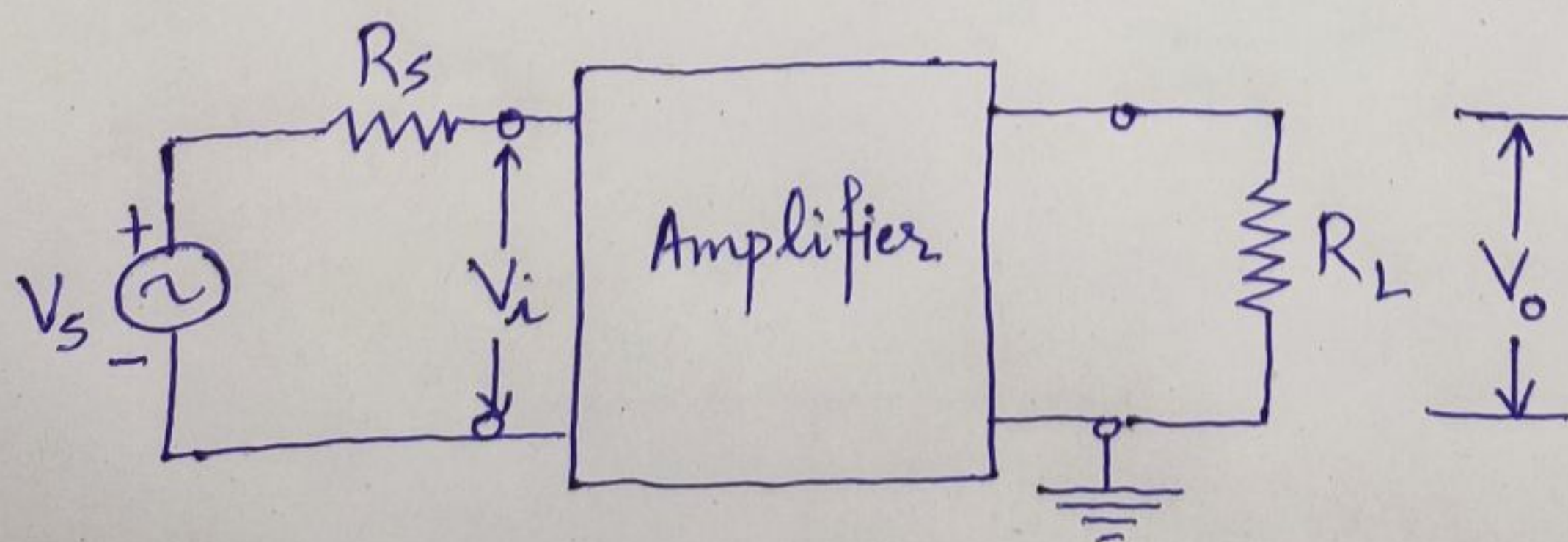


Fig. 1. (a) Basic Voltage Amplifier



Figure 1. (b) shows a Thevenin's equivalent circuit of a voltage amplifier. (2)

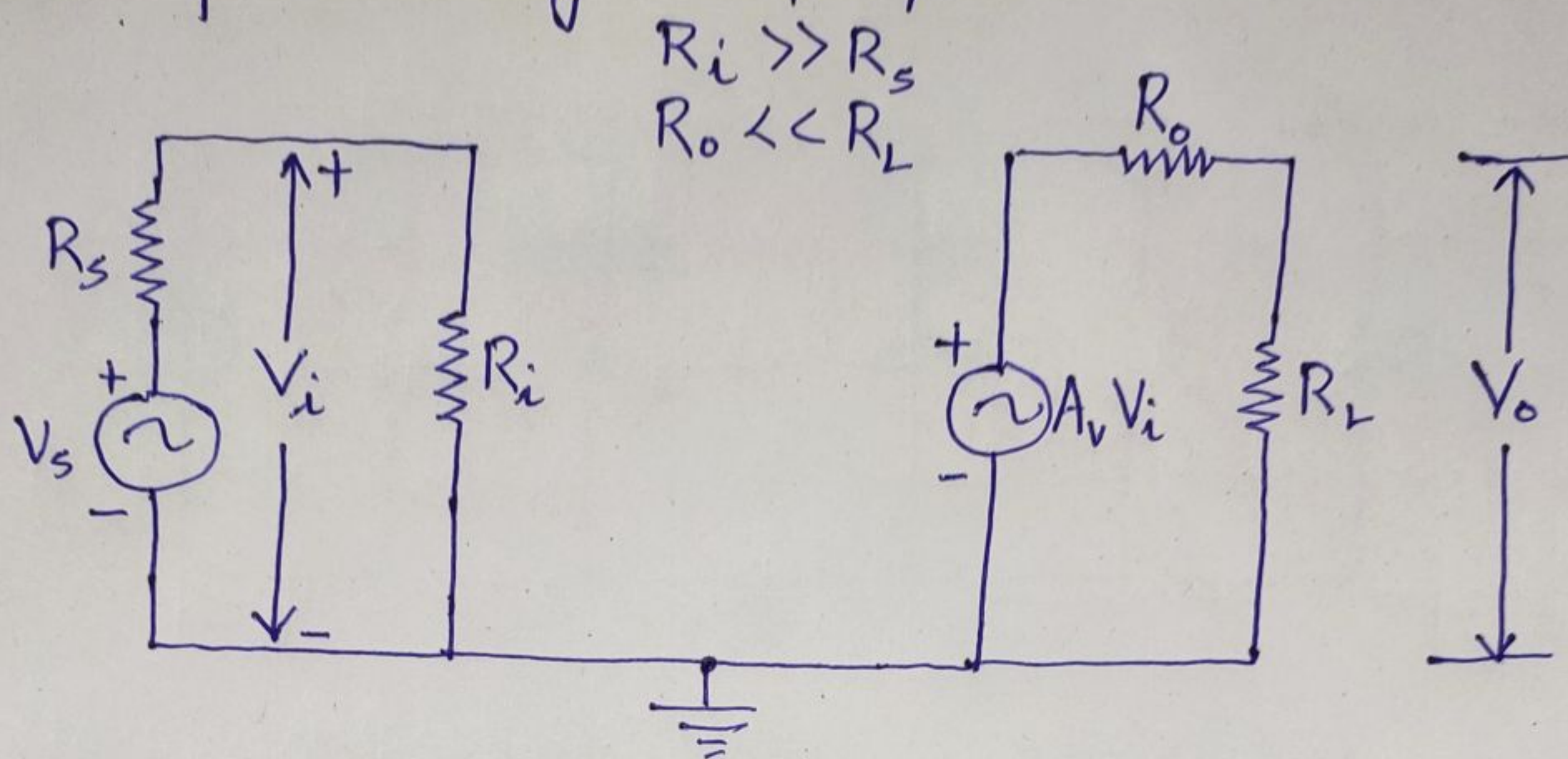


Figure 1. (b). Thevenin's equivalent

Since,  $R_i \gg R_s$ , then  $V_i \approx V_s$ .

Also,  $R_L \gg R_o$ , then  $V_o \approx A_v V_i \approx A_v V_s$

Note:  $R_i = \text{Amplifier input resistance}$   
 $R_o = \text{Amplifier output resistance}$

An ideal voltage amplifier must have infinite input resistance  $R_i$  and Zero output resistance  $R_o$ . ' $A_v$ ' represents the open-circuit voltage gain with  $R_L = \infty$ .

## 2. Current Amplifier

A current amplifier is represented by a two port network. It is driven by a current source  $I_s$  with source resistance  $R_s$ .

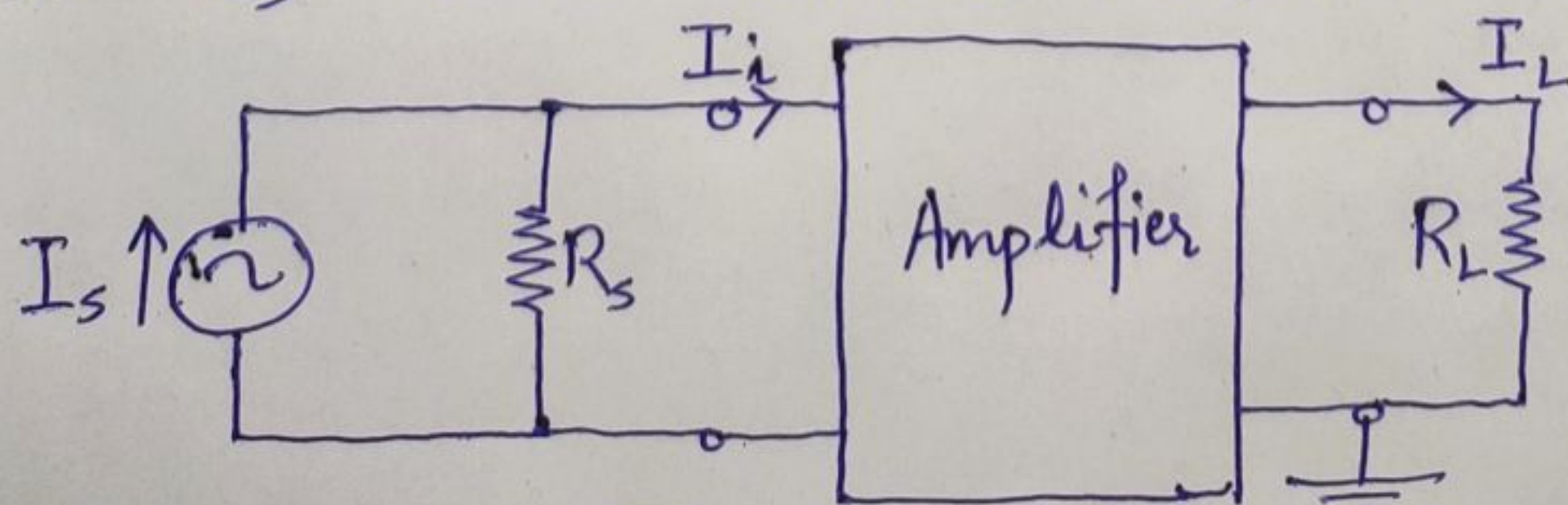


Fig. 2. (a) Basic Current Amplifier



Figure 2 (b) shows a Norton's equivalent circuit of current amplifier. (3)

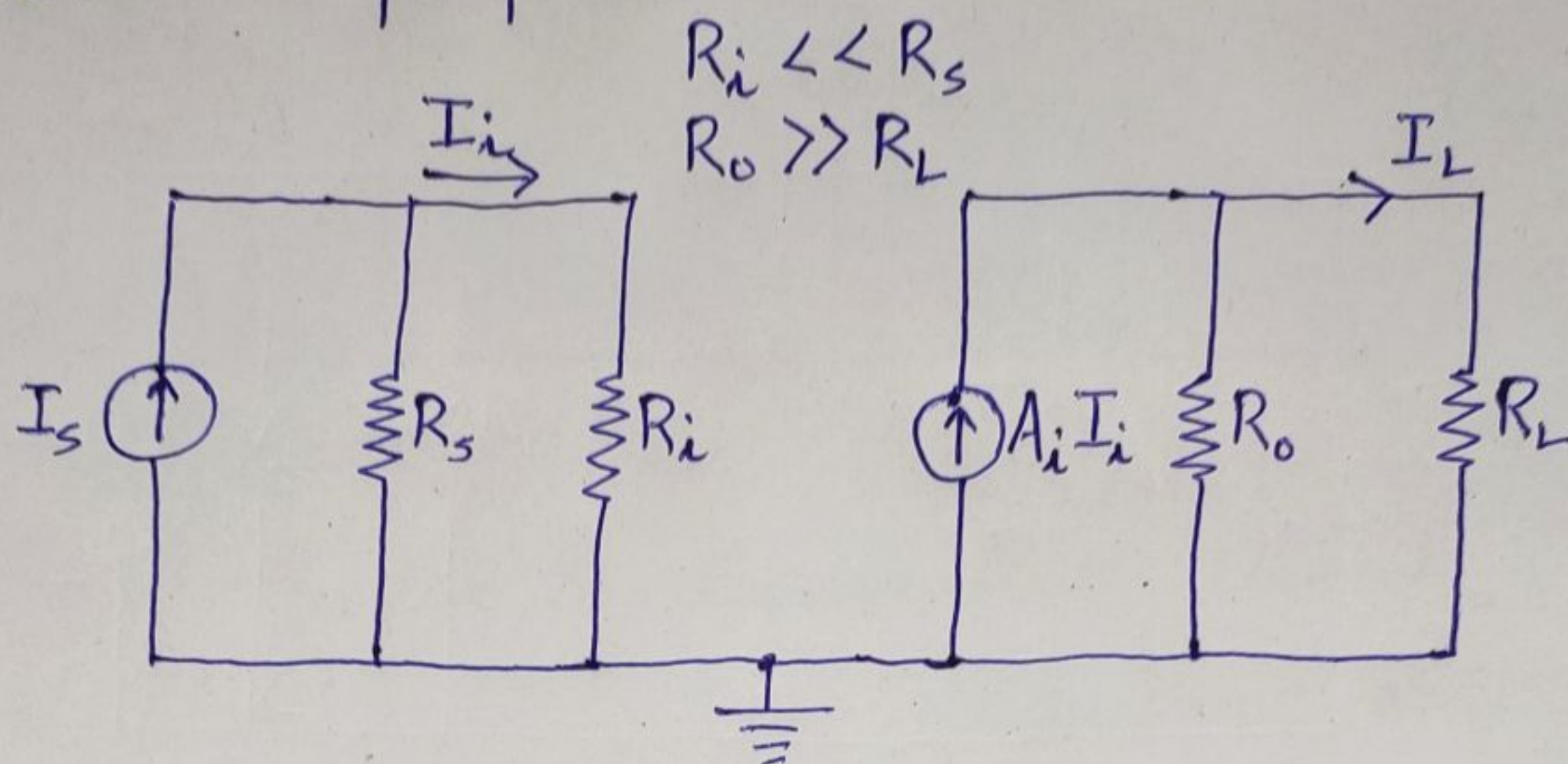


Figure 2 (b). Norton's equivalent

Here  $A_i$  represents short-circuit current gain with  $R_L = 0$ .

$$\therefore A_i \approx \frac{I_L}{I_i}$$

In practice, the current amplifier has low input resistance and high output resistance.

$$\text{i.e. } R_i \ll R_s \text{ and } R_o \gg R_L$$

An ideal current amplifier must have zero input resistance ( $R_i$ ) and infinite output resistance  $R_o$ .

### 3. Transconductance Amplifier

Figure 3. shows the equivalent circuit of a transconductance amplifier in which source is represented by its Thevenin's equivalent and amplifier is represented by its Norton's equivalent circuit.



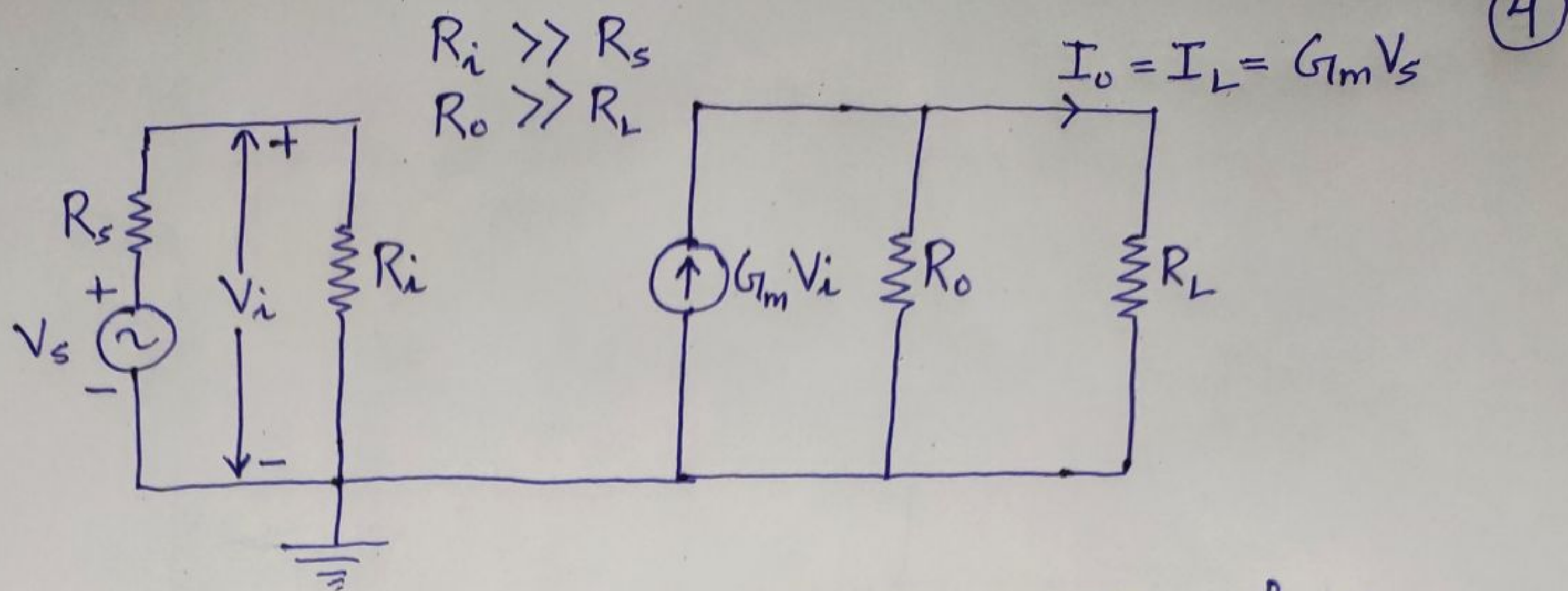


Figure 3. Equivalent circuit for Transconductance amplifier

An ideal transconductance amplifier provides an output current which is proportional to the input signal voltage and is independent of  $R_s$  and  $R_L$ . The ideal transconductance amplifier must have  $R_i = \infty$  and  $R_o = \infty$ .

$$\therefore I_L \approx G_m V_i \approx G_m V_s$$

where ' $G_m$ ' represents the short circuit mutual conductance or transfer conductance.

Note that for transconductance amplifier,

$$R_i \gg R_s \text{ and } R_o \gg R_L.$$

#### 4. Transresistance Amplifier

Figure 4. shows the equivalent circuit of a transresistance amplifier in which source is represented by its Norton's equivalent and amplifier is represented by its Thevenin's equivalent.



(5)

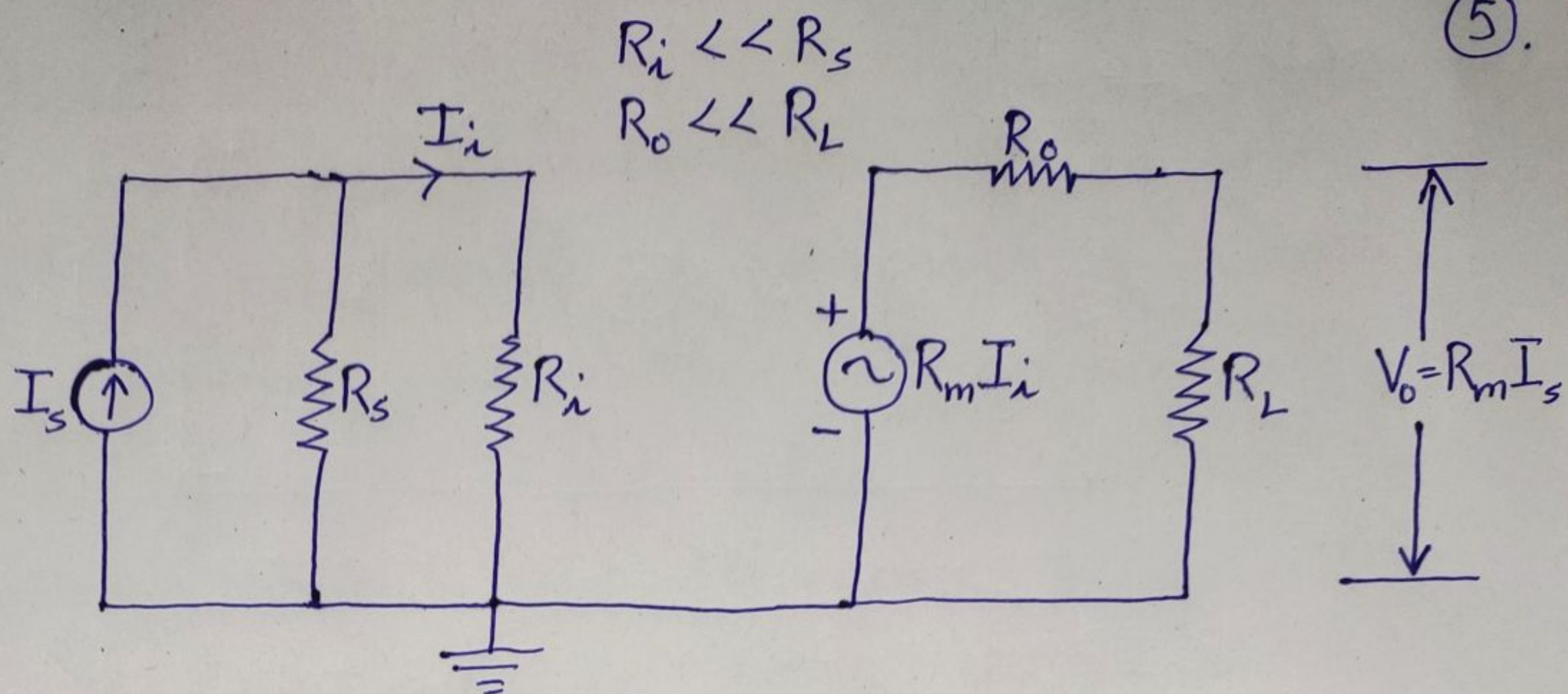


Figure 4. Equivalent circuit for Transresistance amplifier

The output voltage  $V_o$  is proportional to the signal current  $I_s$ , independent of the magnitudes of  $R_s$  and  $R_L$ .

Since  $R_s \gg R_i$ ,  $I_i \approx I_s$ .

Also  $R_o \ll R_L$ , then  $V_o \approx R_m I_i \approx R_m I_s$

Note that,  $R_m = \frac{V_o}{I_i}$  with  $R_L = \infty$

where ' $R_m$ ' is the open-circuit transfer resistance.

---