

## Voltage - Series Feedback Amplifier

①

The schematic diagram of the voltage-series feedback amplifier is shown in Figure 1. The op-amp is represented by its schematic symbol, including its large-signal voltage gain  $A$ , and the feedback circuit is composed of two resistors,  $R_i$  and  $R_F$ .

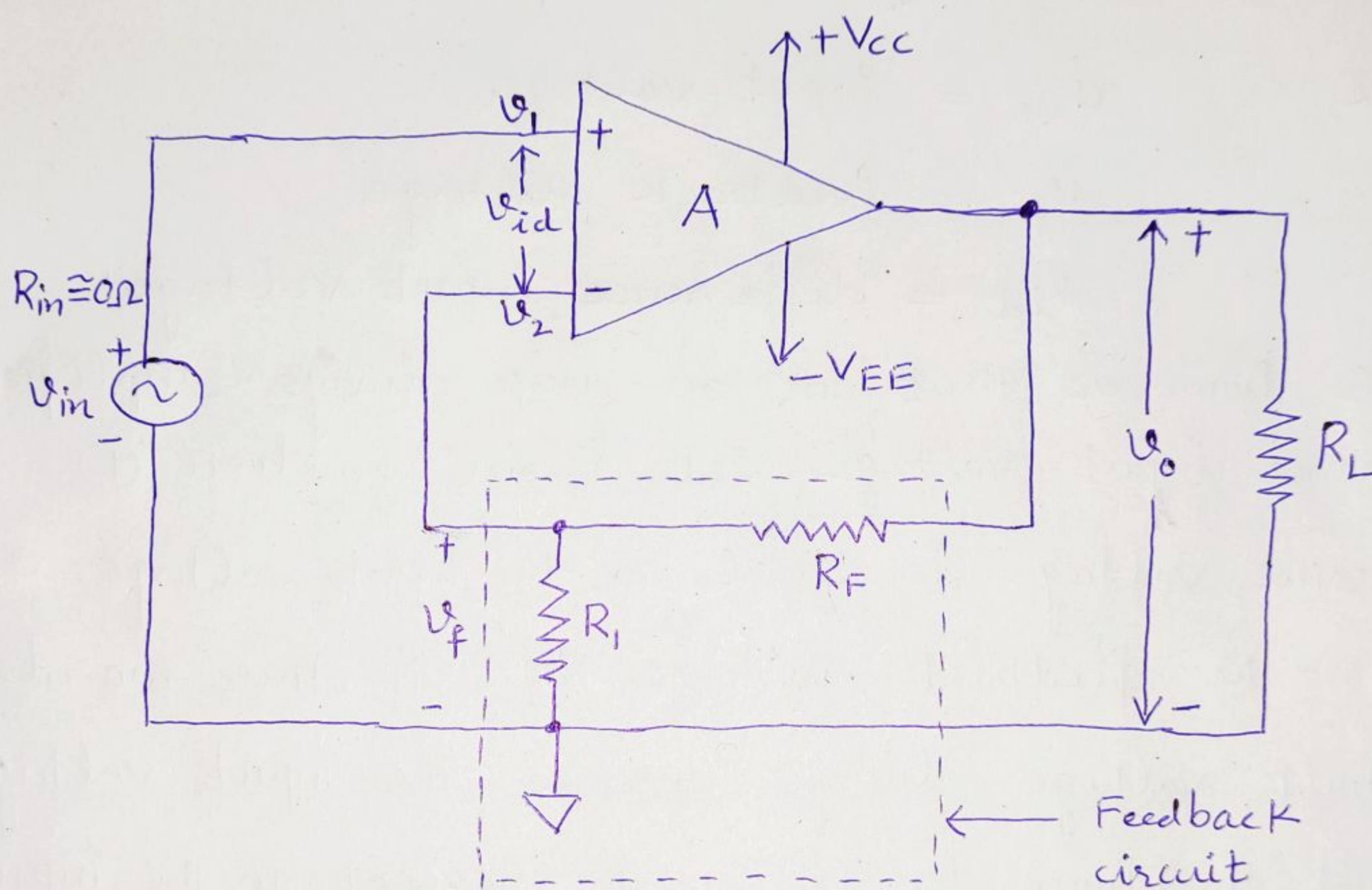


Figure 1: Voltage - Series Feedback Amplifier  
(Non-inverting amplifier with feedback)

The circuit shown in Figure 1 is commonly known as a noninverting amplifier with feedback (or closed-loop noninverting amplifier) because it uses feedback, and the input signal is applied to the noninverting input terminal of the op-amp.

Before proceeding, it is necessary to define some important terms for the voltage-series feedback amplifier.

Open-loop voltage gain (or gain without feedback)  $A = \frac{V_o}{V_{id}}$



closed-loop voltage gain (or gain with feedback)  $A_F = \frac{V_o}{V_{in}}$  (2)

Gain of the feedback circuit,  $B = \frac{V_f}{V_o}$

### Negative Feedback

Referring to the circuit of Figure 1, Kirchhoff's voltage equation for the input loop is,

$$V_{id} = V_{in} - V_f \quad \text{--- (1)}$$

where

$V_{in}$  = input voltage

$V_f$  = feedback voltage

$V_{id}$  = difference input voltage

Recall, however, that an op-amp always amplifies the difference input voltage  $V_{id}$ . From equation (1), this difference voltage is equal to the input voltage  $V_{in}$  minus the feedback voltage  $V_f$ . In other words, the feedback voltage always opposes the input voltage (or is out of phase by  $180^\circ$  with respect to the input voltage); hence the feedback is said to be negative.

### Closed-Loop Voltage Gain

As defined previously, the closed-loop voltage gain is,

$$A_F = \frac{V_o}{V_{in}}$$

However, by output equation of op-amp,

$$V_o = A(V_1 - V_2)$$

Referring to Figure 1, we see that

$$V_1 = V_{in}$$



$$v_2 = v_f = \frac{R_1 v_o}{R_1 + R_F}$$

Since  $R_i \gg R_1$

(3)

Therefore,

$$v_o = A \left( v_{in} - \frac{R_1 v_o}{R_1 + R_F} \right)$$

Rearranging, we get

$$v_o = \frac{A(R_1 + R_F) v_{in}}{R_1 + R_F + AR_1}$$

Thus

$$A_F = \frac{v_o}{v_{in}} = \frac{A(R_1 + R_F)}{R_1 + R_F + AR_1} \quad \text{--- (2)}$$

Generally,  $A$  is very large (typically  $10^5$ ). Therefore,

$$AR_1 \gg (R_1 + R_F) \text{ and } (R_1 + R_F + AR_1) \cong AR_1$$

Thus,

$$A_F = \frac{v_o}{v_{in}} = 1 + \frac{R_F}{R_1} \quad \text{--- (3)}$$

Equation (3) is important because it shows that the gain of the voltage-series feedback amplifier is determined by the ratio of two resistors,  $R_1$  and  $R_F$ .

As defined previously, the gain of the feedback circuit (B) is the ratio of  $v_f$  and  $v_o$ . Referring to Figure 1, this gain is

$$B = \frac{v_f}{v_o}$$

$$B = \frac{R_1}{R_1 + R_F} \quad \text{--- (4)}$$

Comparing equations (3) and (4), we can conclude that

$$A_F = \frac{1}{B} \quad \text{--- (5)}$$



This means that the gain of the feedback circuit (4) is the reciprocal of the closed-loop voltage gain. In other words, for given  $R_1$  and  $R_F$ , the values of  $A_F$  and  $B$  are fixed.

Finally, the closed-loop voltage gain  $A_F$  can be expressed in terms of open-loop gain  $A$  and feedback circuit gain  $B$  as follows. Rearranging equation (2)

$$A_F = \frac{A \left( \frac{R_1 + R_F}{R_1 + R_F} \right)}{\frac{R_1 + R_F}{R_1 + R_F} + \frac{A R_1}{R_1 + R_F}}$$

Using equation (4) yields

$$A_F = \frac{A}{1 + AB} \quad \text{--- (6)}$$

where  $A_F$  = closed-loop voltage gain

$A$  = open-loop voltage gain

$B$  = gain of the feedback circuit

$AB$  = loop gain

A one-line block diagram of equation (6) is shown in Figure 2.

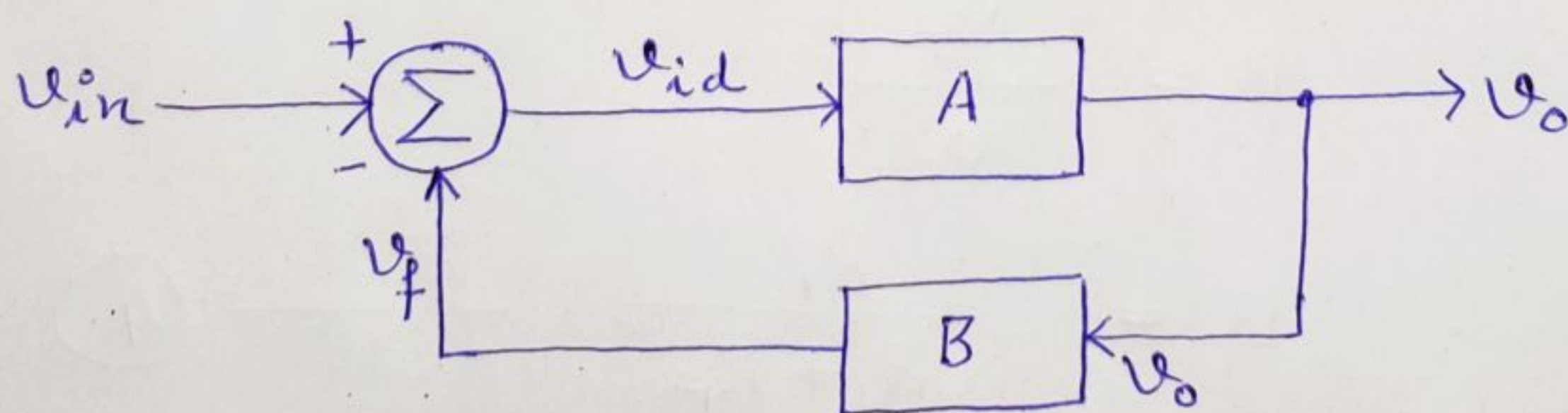


Figure 2. Block diagram representation of noninverting amplifier with feedback.



This block diagram illustrates a standard form for representing a system with feedback and also indicates the relationship between different variables of the system. (5)

### Input Resistance with Feedback

Figure 3. shows a voltage series feedback amplifier with the op-amp equivalent circuit. In this circuit  $R_i$  is the input resistance (open loop) of the op-amp, and  $R_{if}$  is the input resistance of the amplifier with feedback.

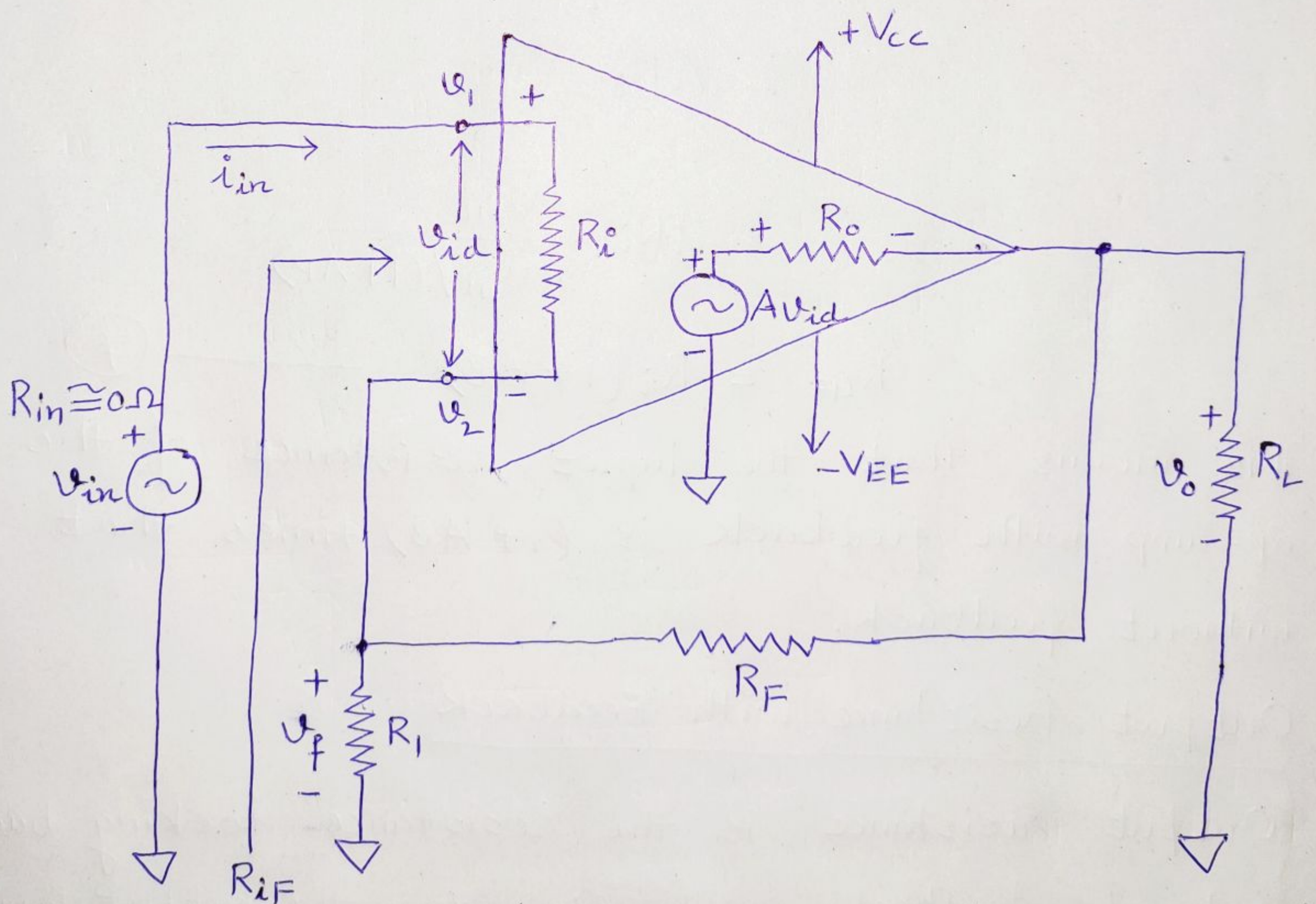


Figure 3. Derivation of input resistance with feedback.



The input resistance with feedback is defined (6)  
as

$$R_{iF} = \frac{V_{in}}{i_{in}} \\ = \frac{V_{in}}{V_{id}/R_i}$$

However,

$$V_{id} = \frac{V_o}{A} \quad \text{and} \quad V_o = \frac{A}{1+AB} V_{in}$$

$$\left[ \text{Note } A = \frac{V_o}{V_{id}} \quad \text{and} \quad A_F = \frac{V_o}{V_{in}} = \frac{A}{1+AB} \right]$$

Therefore,

$$R_{iF} = R_i \frac{V_{in}}{V_o/A} \\ = AR_i \frac{V_{in}}{V_o}$$

$$= AR_i \frac{V_{in}}{A V_{in}/(1+AB)}$$

$$R_{iF} = R_i(1+AB) \quad \text{————— (7)}$$

This means that the input resistance of the op-amp with feedback is  $(1+AB)$  times that without feedback.

### Output Resistance with Feedback

Output resistance is the resistance looking back into the feedback amplifier from the output terminal as shown in Figure 4. This resistance can be obtained by using Thevenin's theorem for dependent



Sources. Specifically, to find output resistance with feedback  $R_{OF}$ , reduce independent source  $V_{in}$  to zero, apply an external voltage  $V_o$ , and then calculate the resulting current  $i_o$ . In short, the  $R_{OF}$  is defined as follows:

$$R_{OF} = \frac{V_o}{i_o} \quad \text{--- (8)}$$

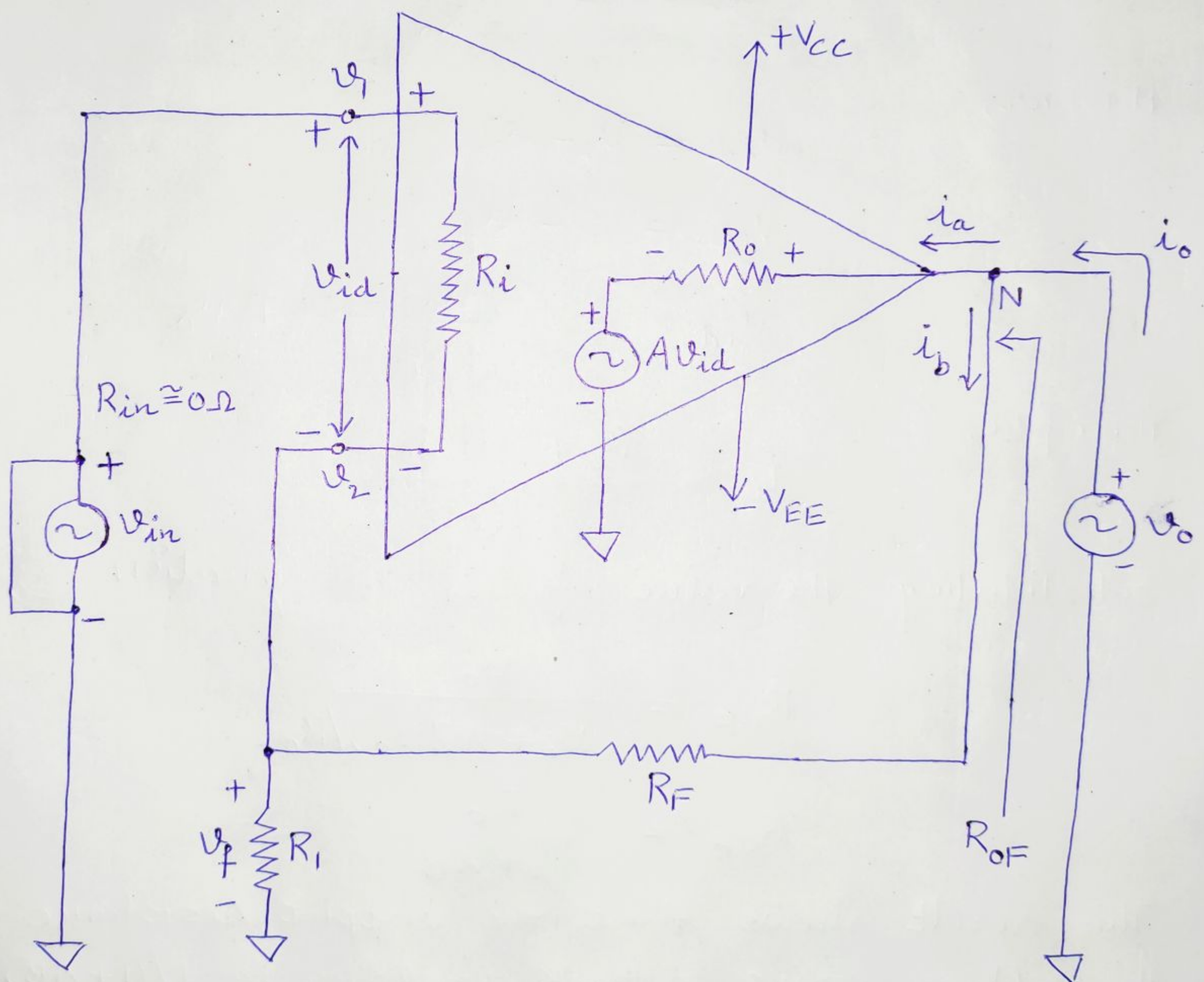


Figure 4. Derivation of output resistance with feedback.

Writing Kirchhoff's current equation at output node N, we get



$$i_o = i_a + i_b$$

Since  $[(R_F + R_i) \parallel R_i] \gg R_o$  and  $i_a \gg i_b$ ,

$$\text{Therefore, } i_o \cong i_a$$

The current  $i_o$  can be found by writing Kirchhoff's voltage equation for the output loop:

$$V_o - R_o i_o - A V_{id} = 0$$

$$i_o = \frac{V_o - A V_{id}}{R_o}$$

However,

$$V_{id} = V_1 - V_2$$

$$V_{id} = 0 - V_f$$

$$V_{id} = - \frac{R_i V_o}{R_i + R_F} = -B V_o$$

Therefore,

$$i_o = \frac{V_o + AB V_o}{R_o}$$

Substituting the value of  $i_o$  in equation (8),

$$R_{oF} = \frac{V_o}{(V_o + AB V_o)/R_o}$$

$$R_{oF} = \frac{R_o}{1 + AB}$$

This result shows that the output resistance of the voltage-series feedback amplifier is  $1/(1+AB)$  times the output resistance  $R_o$  of the op-amp. i.e. the output resistance of the op-amp with feedback is much smaller than the output resistance without feedback.