

### Output Resistance with Feedback

The output resistance with feedback  $R_{OF}$  is the resistance measured at the output terminal of the feedback amplifier. The output resistance of the noninverting amplifier was obtained by using Thevenin's theorem, and we can do the same for the inverting amplifier. Thevenin's equivalent circuit for  $R_{OF}$  of the inverting amplifier is shown in Figure 4. Note that this Thevenin's equivalent circuit is exactly the same as that for noninverting amplifier because the output resistance  $R_{OF}$  of the inverting amplifier must be identical to that of the noninverting amplifier.

i.e.  $R_{OF} = \frac{R_o}{1 + AB}$  ————— (8)

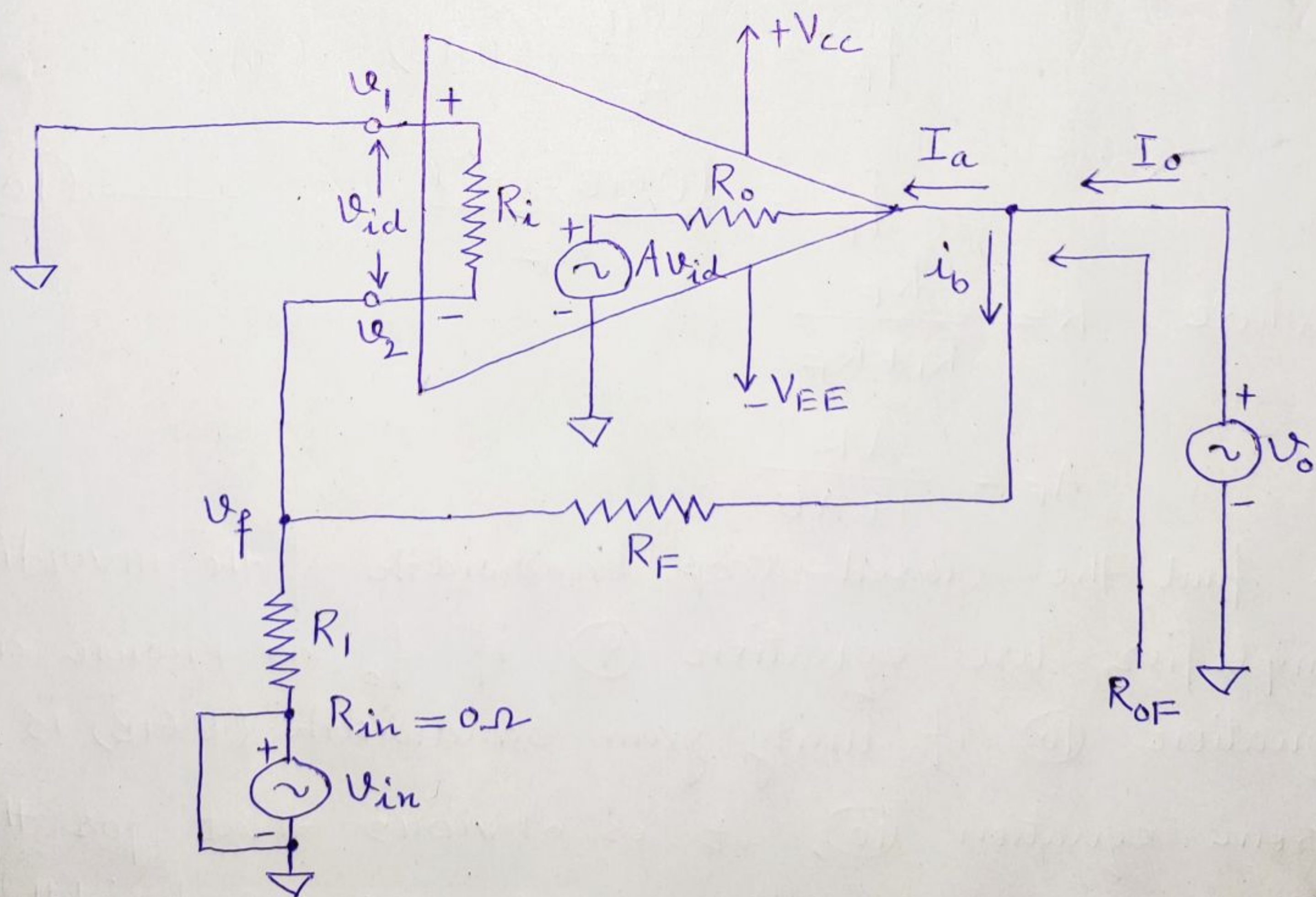


Figure 4. Thevenin's equivalent circuit for  $R_{OF}$  of the inverting amplifier.



## Bandwidth with Feedback

(8)

The gain-bandwidth product of a single break frequency op-amp is always constant. We also saw that the gain of the amplifier with feedback is always less than the gain without feedback. Therefore, the bandwidth of the amplifier with feedback  $f_F$  must be larger than that without feedback.

$$f_F = f_o (1 + AB) \quad \text{--- (9)}$$

where  $f_o$  = break frequency of the op-amp  
=  $\frac{\text{Unit gain bandwidth}}{\text{open-loop voltage gain}}$

$$f_o = \frac{UGB}{A} \quad \left[ \begin{array}{l} \text{true only for the single break} \\ \text{frequency op-amp as 741} \end{array} \right]$$

Substituting the value of  $f_o$  in equation - (9), we get

$$f_F = \frac{UGB}{A} (1 + AB)$$

$$f_F = \frac{(UGB).(K)}{A_F} \quad \text{--- (10)}$$

where  $K = \frac{R_F}{R_i + R_F}$

$$A_F = \frac{AK}{1 + AB}$$

To find the closed-loop bandwidth of the inverting amplifier, use equation (9) if  $f_o$  is known and use equation (10) if unity gain-bandwidth (UGB) is given.

From equation (10), it is obvious that for the same closed loop gain, the closed loop bandwidth for



the inverting amplifier is lower than that for ⑨ the noninverting amplifier by a factor of  $K (< 1)$ . For example, when the closed loop gain is equal to 1, the bandwidths will be

$f_F = UGB$  for the noninverting amplifier and

$$f_F = \frac{UGB}{2} \text{ for the inverting amplifier, since } R_1 = R_F.$$

However, as the closed-loop gain  $A_F$  approaches the open-loop gain  $A$ , the difference between the noninverting and inverting amplifier bandwidths approaches zero. As an extreme limit, when  $K \cong 1$ , the value of  $f_F$  for both the noninverting and inverting amplifiers is approximately the same.

### Total Output Offset Voltage with Feedback

When the temperature and power supply voltages are fixed, the output offset voltage is a function of the gain of an op-amp. However, we saw that the gain of the op-amp with feedback is always less than that without feedback. Therefore, the output offset voltage with feedback  $V_{OOT}$  must always be smaller than that without feedback. Therefore,

$$\text{Total output offset voltage with feedback} = \frac{\text{Total output offset voltage without feedback}}{1 + AB}$$



i.e.

$$V_{OOT} = \frac{\pm V_{sat}}{1 + AB}$$

————— (11)

(10)

where  $\pm V_{sat}$  = Saturation voltage

$A$  = open-loop voltage gain of the op-amp

$B$  = gain of the feedback circuit

The output voltage of the op-amp without feedback can be either  $+V_{sat}$  or  $-V_{sat}$  because of its very high voltage gain  $A$ , which is typically of the order of  $10^5$ .

Note that the  $V_{OOT}$  equation for the inverting amplifier is the same as that for the noninverting amplifier.

This is because, when the input signal  $V_{in}$  is reduced to zero, both inverting and noninverting amplifiers result in the same circuit.

In addition, because of the negative feedback, the effect of noise, variations in supply voltages, and changes in temperature on the output voltage of the inverting amplifiers are significantly reduced.

Finally, the two special cases of the inverting amplifier with feedback are the current-to-voltage converter and the inverter.



## Current-to-Voltage Converter

(11)

Let us reconsider the ideal voltage-gain equation of the inverting amplifier,

$$\frac{V_o}{V_{in}} = -\frac{R_F}{R_1}$$

Therefore,

$$V_o = -\left(\frac{V_{in}}{R_1}\right)R_F$$

However, since  $V_1 = 0V$  and  $V_1 = V_2$

$$\therefore \frac{V_{in}}{R_1} = i_{in}$$

and

$$V_o = -i_{in}R_F$$

This means that if we replace the  $V_{in}$  and  $R_1$  combination by a current source  $i_{in}$  as shown in Figure 5, the output voltage  $V_o$  becomes proportional to the input current  $i_{in}$ . In other words, the circuit of Figure 5 converts the input current into a proportion output voltage.

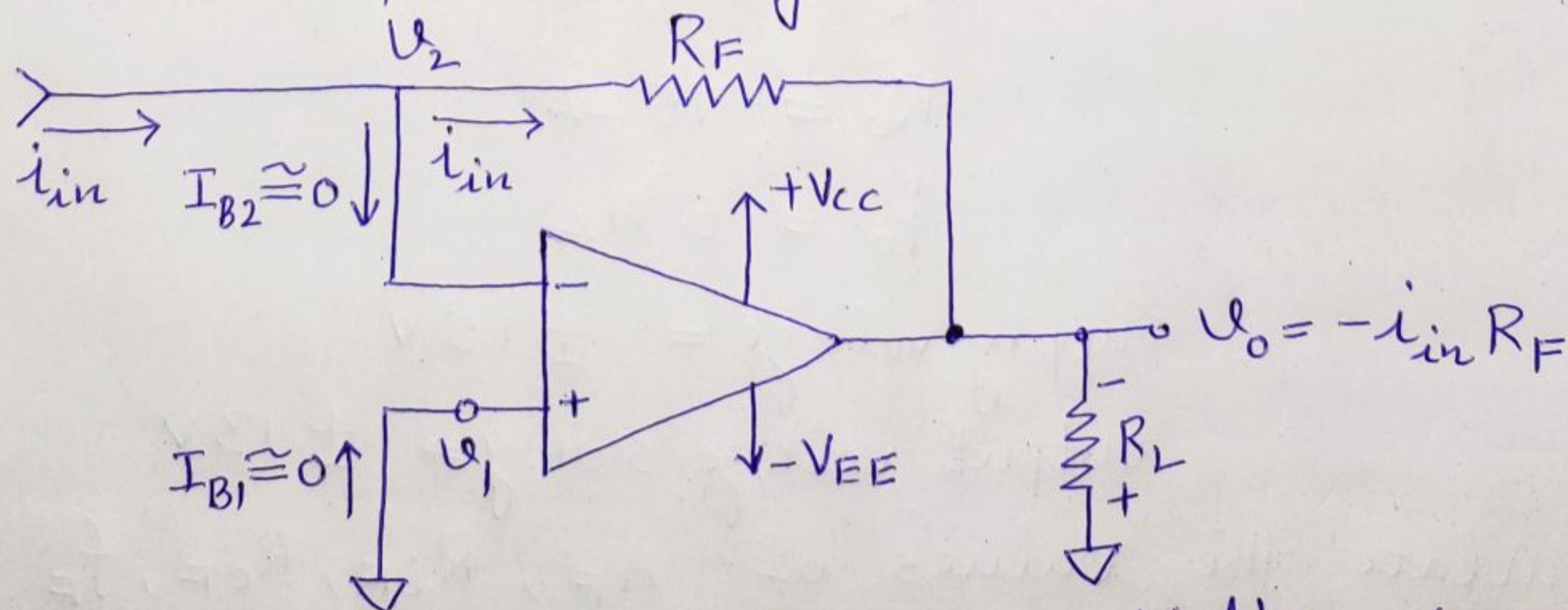


Figure 5. Current-to-Voltage Converter



One of the most common uses of the current-to-voltage converter is in sensing current from photo-detectors. (12)

### Inverter

If we need an output signal equal in amplitude but opposite in phase to that of the input signal, we can use the inverter. The inverting amplifier with feedback works as an inverter if  $R_1 = R_F$ . Since the inverter is a special case of the inverting amplifier, all the equations developed for the inverting amplifier are also applicable here. The equations can be applied by merely substituting  $(A/2)$  for  $(1+AB)$ , since  $B = \frac{1}{2}$ .

Q1. For the inverting amplifier,  $R_1 = 470\Omega$  and  $R_F = 4.7\text{ K}\Omega$ . Assume that the op-amp is the 741 having the specifications given as:

$$A = 200000$$

$$R_i = 2\text{ M}\Omega$$

$$R_o = 75\Omega$$

$$f_o = 5\text{ Hz}$$

$$\text{Supply voltage} = \pm 15\text{ V}$$

$$\text{output voltage swing} = \pm 13\text{ V}$$

Calculate the values of  $A_F$ ,  $R_{iF}$ ,  $R_{oF}$ ,  $f_F$  and  $V_{oot}$ .



Solution: Using the given values of  $R_1$  and  $R_F$ ,

(13)

$$K = \frac{R_F}{R_1 + R_F} = \frac{4700}{470 + 4700} = \frac{1}{1.1}$$

$$B = \frac{R_1}{R_1 + R_F} = \frac{470}{470 + 4700} = \frac{1}{11}$$

and

$$1 + AB = \left[ 1 + (2 \times 10^5) \left( \frac{1}{11} \right) \right] = 18182.8$$

Therefore the values of the closed-loop parameters are

$$A_F = - \frac{AK}{1 + AB}$$

$$\therefore, A_F = - \frac{200000 \times (1/1.1)}{18182.8} = -10$$

$$R_{iF} = R_1 + \left( \frac{R_F}{1 + A} \parallel R_i \right)$$

$$\therefore, R_{iF} = 470 + \left[ \frac{4700}{200000} \parallel 2 \times 10^6 \right]$$

$$R_{iF} = 470 \Omega$$

$$R_{oF} = \frac{R_o}{1 + AB} = \frac{75}{18182.8} = 4.12 \text{ m}\Omega$$

$$f_F = \frac{(UGB)(K)}{A_F} = \frac{f_o \cdot A \cdot K}{A_F}$$

$$f_F = f_o \cdot A \cdot \frac{(1 + AB)}{A} = f_o (1 + AB)$$

$$= 5 \times 18182.8 = 90.9 \text{ KHz}$$



$$V_{OOT} = \frac{\pm 13V}{18182.8} = \pm 0.715mV.$$

---

(14)