

## Voltage - Controlled Oscillator

①

In the preceding oscillators, the frequency is determined by the RC time constant. However, there are applications, such as frequency modulation (FM), tone generators, and frequency shift keying (FSK), where the frequency needs to be controlled by means of an input voltage called control voltage. This function is achieved in the voltage-controlled oscillator (VCO), also called a voltage-to-frequency converter. A typical example is the Signetics NE/SE 566 VCO, which provides simultaneous square wave and triangular wave outputs as a function of input voltage. Figure 1 is a block diagram of the 566.

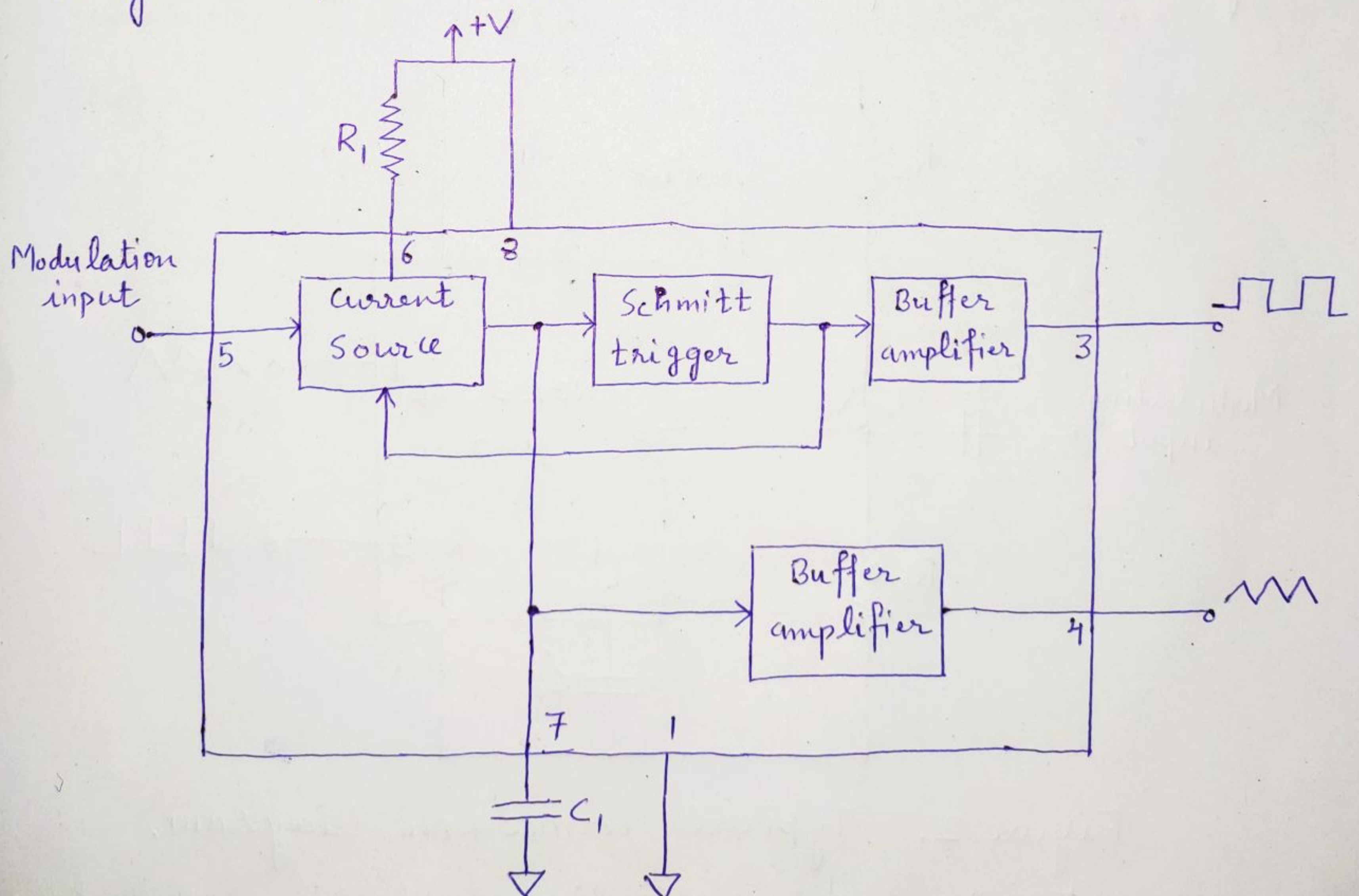


Figure 1. Block diagram of VCO 566.



The frequency of oscillation is determined by an external resistor  $R_1$ , capacitor  $C_1$ , and the voltage  $V_c$  applied to the control terminal 5. The triangular wave is generated by alternately charging the external capacitor  $C_1$  by one current source and then linearly discharging it by another. The charge-discharge levels are determined by Schmitt trigger action. The Schmitt trigger also provides the square wave output. The output waveforms are buffered so that the output impedance of each is  $50\ \Omega$ . The typical amplitude of the triangular wave is  $2.4\text{ V}_{pp}$  and that of the square wave is  $5.4\text{ V}_{pp}$ .

Figure 2 is a typical connection diagram. In this

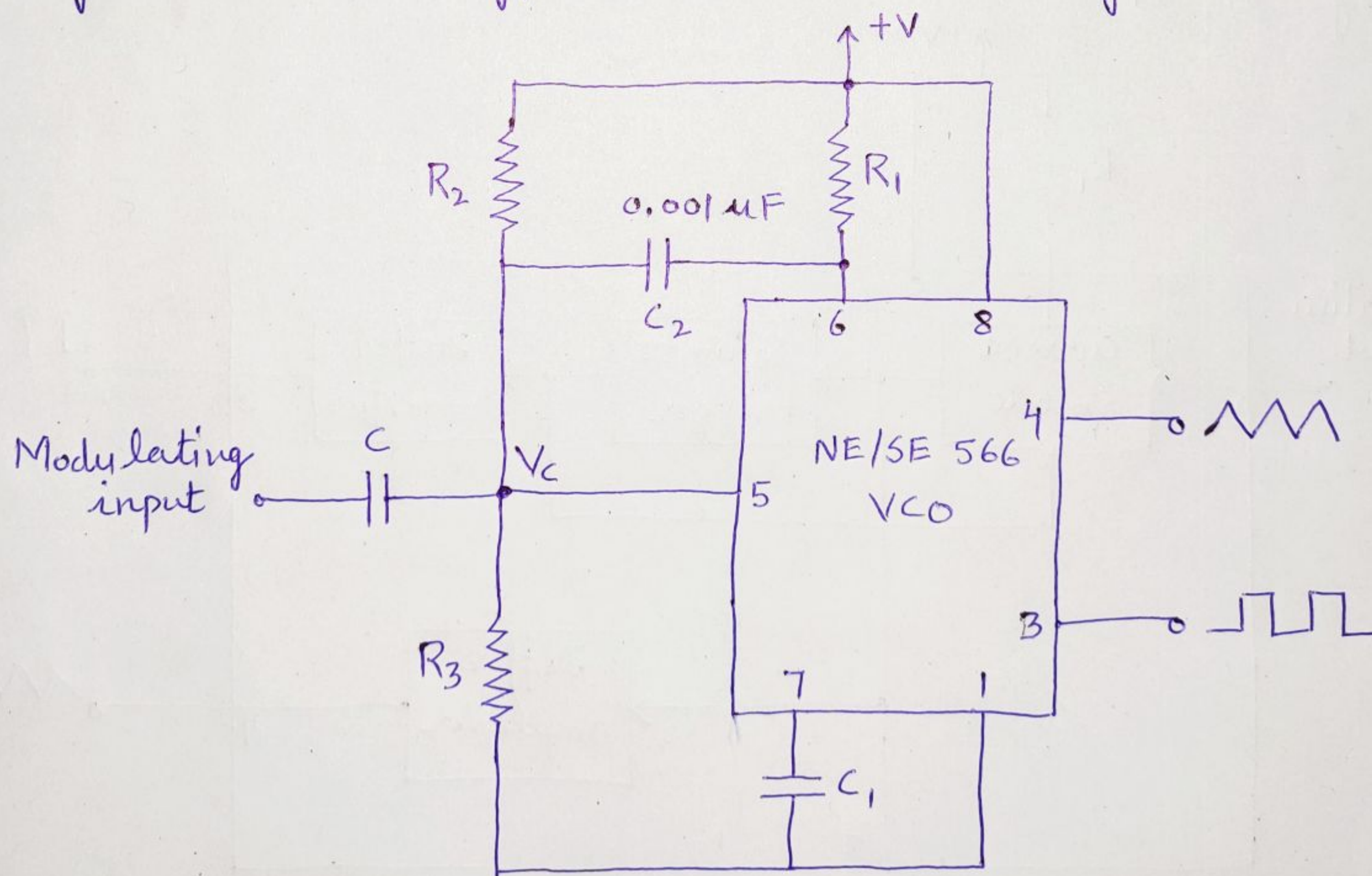


Figure 2. Typical Connection Diagram.

arrangement, the  $R_1 C_1$  combination determines the free running frequency, and the control voltage  $V_c$  at



terminal 5 is set by the voltage divider formed with <sup>(3)</sup>  
 $R_2$  and  $R_3$ . The initial voltage  $V_c$  at terminal 5 must  
be in the range

$$\frac{3}{4} (+V) \leq V_c \leq +V \quad \text{--- (1)}$$

where  $+V$  is the total supply voltage. The modulating  
signal is ac coupled with the capacitor  $C$  and must  
be  $< 3 V_{pp}$ . The frequency of the output waveforms  
is approximated by

$$f_o \cong \frac{2 (+V - V_c)}{R_1 C_1 (+V)} \quad \text{--- (2)}$$

where  $R_1$  should be in the range  $2 K\Omega < R_1 < 20 K\Omega$ .  
For a fixed  $V_c$  and constant  $C_1$ , the frequency  $f_o$   
can be varied over a 10:1 frequency range by the  
choice of  $R_1$  between  $2 K\Omega$  and  $20 K\Omega$ . Similarly,  
for a constant  $R_1 C_1$  product, the frequency  $f_o$  can  
be modulated over a 10:1 range by the control  
voltage  $V_c$ . In either case the maximum output frequency  
is 1 MHz. A small capacitor of  $0.001 \mu F$  should be  
connected between pins 5 and 6 to eliminate possible  
oscillations in the control current source.

---



## Comparators and Converters

(4)

A comparator, as its name implies, compares a signal voltage on one input of an op-amp with a known voltage called the reference voltage on the other input. In its simplest form, it is nothing more than an open loop op-amp, with two analog inputs and a digital output; the output may be (+) or (-) saturation voltage, depending on which input is the larger. Comparators are used in circuits such as digital interfacing, Schmitt triggers, discriminators, voltage-level detectors, and oscillators.

### Basic Comparator

Figure 3 shows an op-amp used as a comparator. A fixed reference voltage  $V_{ref}$  of 1V is applied to the (-) input, and the other time-varying signal voltage  $V_{in}$  is applied to the (+) input. Because of this arrangement, the circuit is called the noninverting comparator.

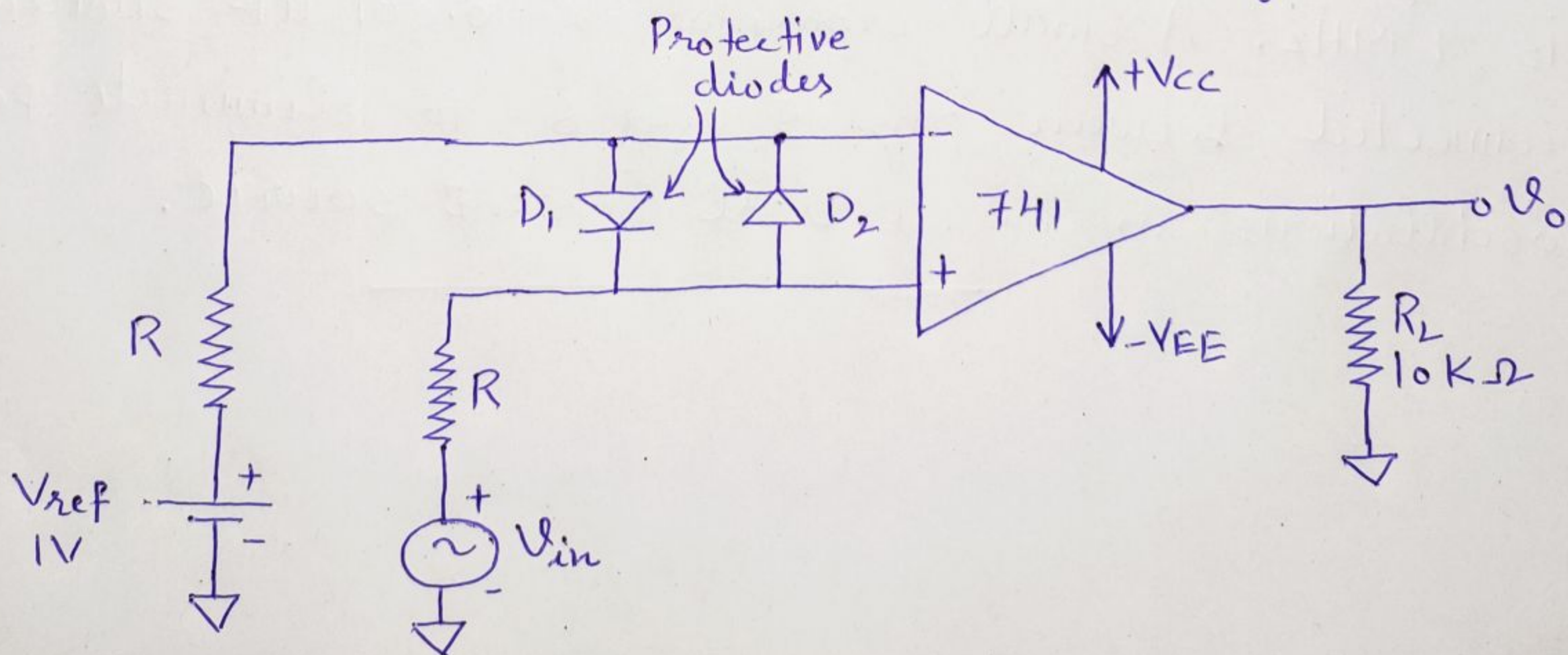


Figure 3. Noninverting Comparator.



When  $V_{in}$  is less than  $V_{ref}$ , the output voltage  $V_o$  is at  $-V_{sat}$  ( $\cong -V_{EE}$ ) because the voltage at the  $(-)$  input is higher than that at the  $(+)$  input. On the other hand, when  $V_{in}$  is greater than  $V_{ref}$ , the  $(+)$  input becomes positive with respect to the  $(-)$  input, and  $V_o$  goes to  $+V_{sat}$  ( $\cong +V_{CC}$ ). Thus  $V_o$  changes from one saturation level to another whenever  $V_{in} \cong V_{ref}$  as shown in Figure 4(a). In short, the comparator is a type of analog-to-digital converter.

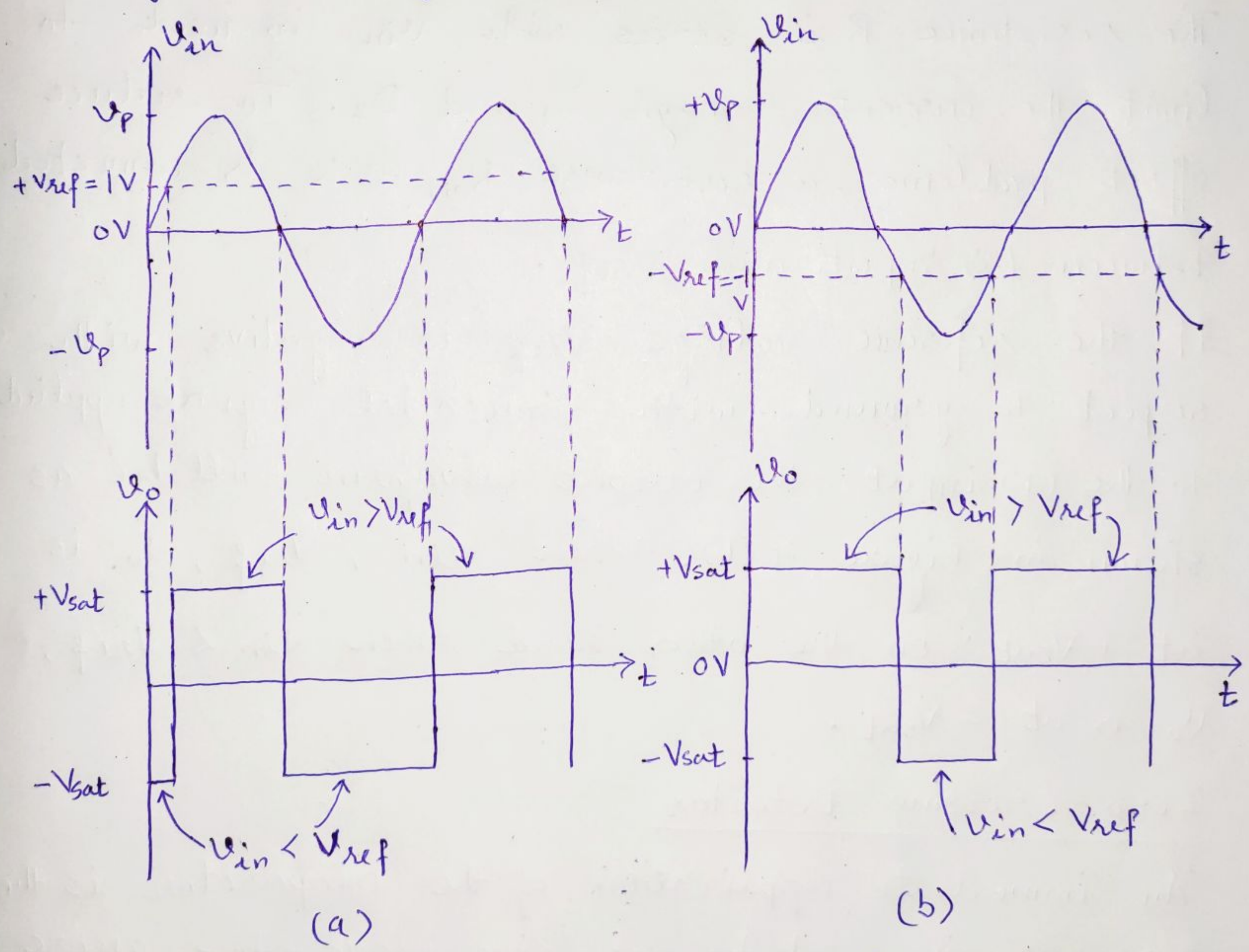


Figure 4. Input and Output waveforms (a) If  $V_{ref}$  is positive (b) If  $V_{ref}$  is negative.

At any given time the  $V_o$  waveform shows whether  $V_{in}$  is greater or less than  $V_{ref}$ . The comparator is



Sometimes also called a voltage-level detector (6) because, for a desired value of  $V_{ref}$ , the voltage level of the input  $V_{in}$  can be detected.

In Figure 3, the diodes  $D_1$  and  $D_2$  protect the op-amp from damage due to excessive input voltage  $V_{in}$ . Because of these diodes, the difference input voltage  $V_{id}$  of the op-amp is clamped to either  $0.7V$  or  $-0.7V$ ; hence the diodes are called clamp diodes. The resistance  $R$  in series with  $V_{in}$  is used to limit the current through  $D_1$  and  $D_2$ . To reduce offset problems, a resistance  $R_{OH} \cong R$  is connected between  $(-)$  input and  $V_{ref}$ .

If the reference voltage  $V_{ref}$  is negative with respect to ground, with sinusoidal signal applied to the  $(+)$  input, the output waveform will be as shown in Figure 4(b). When  $V_{in} > V_{ref}$ ,  $V_o$  is at  $+V_{sat}$ ; on the other hand, when  $V_{in} < V_{ref}$ ,  $V_o$  is at  $-V_{sat}$ .

### Zero Crossing Detector

An immediate application of the comparator is the zero-crossing detector or sine wave-to-square wave converter. The basic comparator of Figure 3 can be used as the zero-crossing detector provided that  $V_{ref}$  is set to zero ( $V_{ref} = 0V$ ). Figure 5



shows the inverting comparator used as a zero-crossing detector. (7)

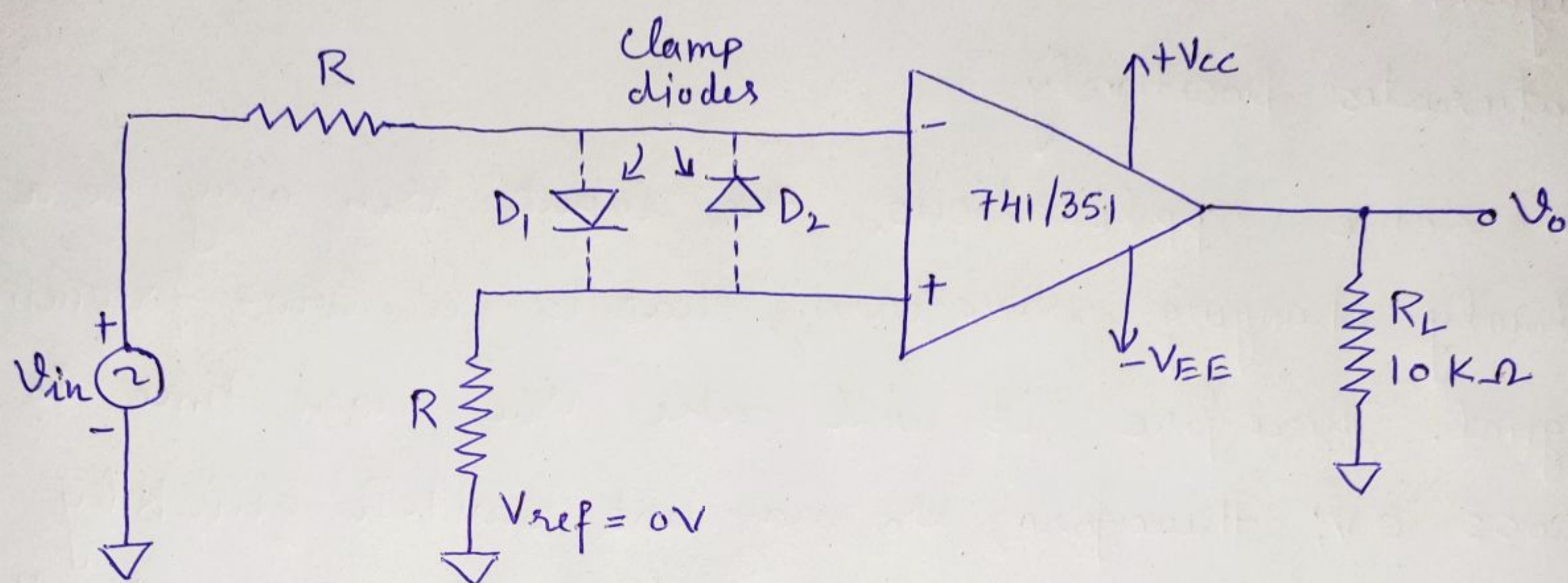


Figure 5. Zero-crossing detector

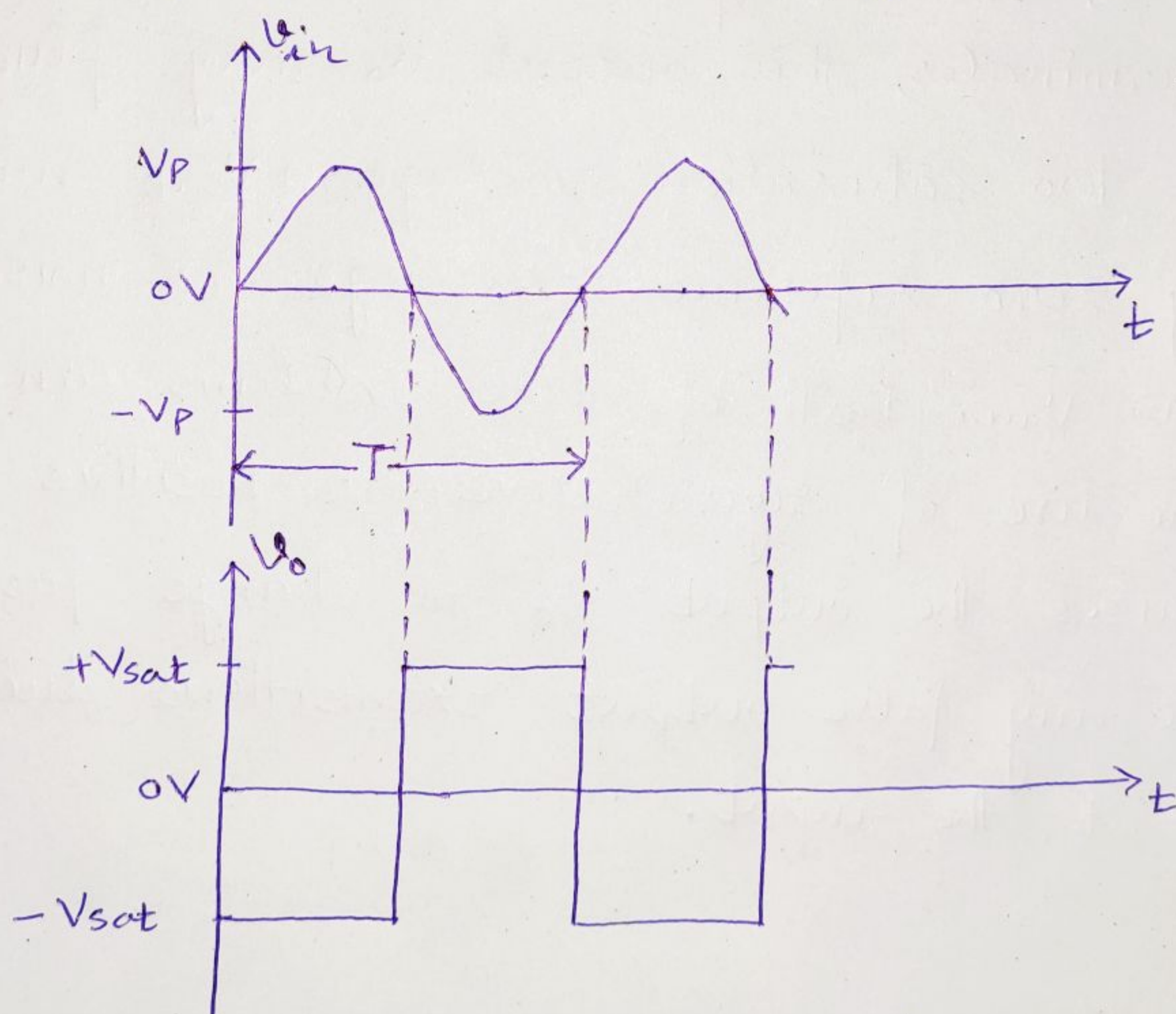


Figure 6. Typical input and output waveforms.

The output voltage  $V_o$  waveform in Figure 6 shows when and in what direction an input signal  $V_{in}$  crosses zero volts. That is, the output  $V_o$  is driven into negative saturation when the input signal  $V_{in}$



passes through zero in the positive direction. ⑧

Conversely, when  $V_{in}$  passes through zero in the negative direction, the output  $V_o$  switches and saturates positively.

In some applications, the input  $V_{in}$  may be a slowly changing waveform, that is, a low-frequency signal. Therefore, it will take  $V_{in}$  more time to cross 0V; therefore,  $V_o$  may not switch quickly from one saturation voltage to the other. On the other hand, because of the noise at the op-amp's input terminals, the output  $V_o$  may fluctuate between two saturation voltage  $+V_{sat}$  and  $-V_{sat}$ , detecting zero reference crossings for noise voltages as well as  $V_{in}$ . Both of these problems can be cured with the use of regenerative or positive feedback that causes the output  $V_o$  to change faster and eliminate any false output transitions due to noise signals at the input.