

## Colpitts Oscillator

①

In the Colpitts oscillator shown in Figure 1,  $Z_1$  and  $Z_2$  are capacitors and  $Z_3$  is an inductor. The resistors  $R_1$ ,  $R_2$  and  $R_E$  provide the necessary dc bias to the transistor.  $C_E$  is a bypass capacitor.  $C_{c1}$  and  $C_{c2}$  are coupling capacitors. The feedback network consisting of capacitors  $C_1$  and  $C_2$  and an inductor  $L$  determines the frequency of the oscillator.

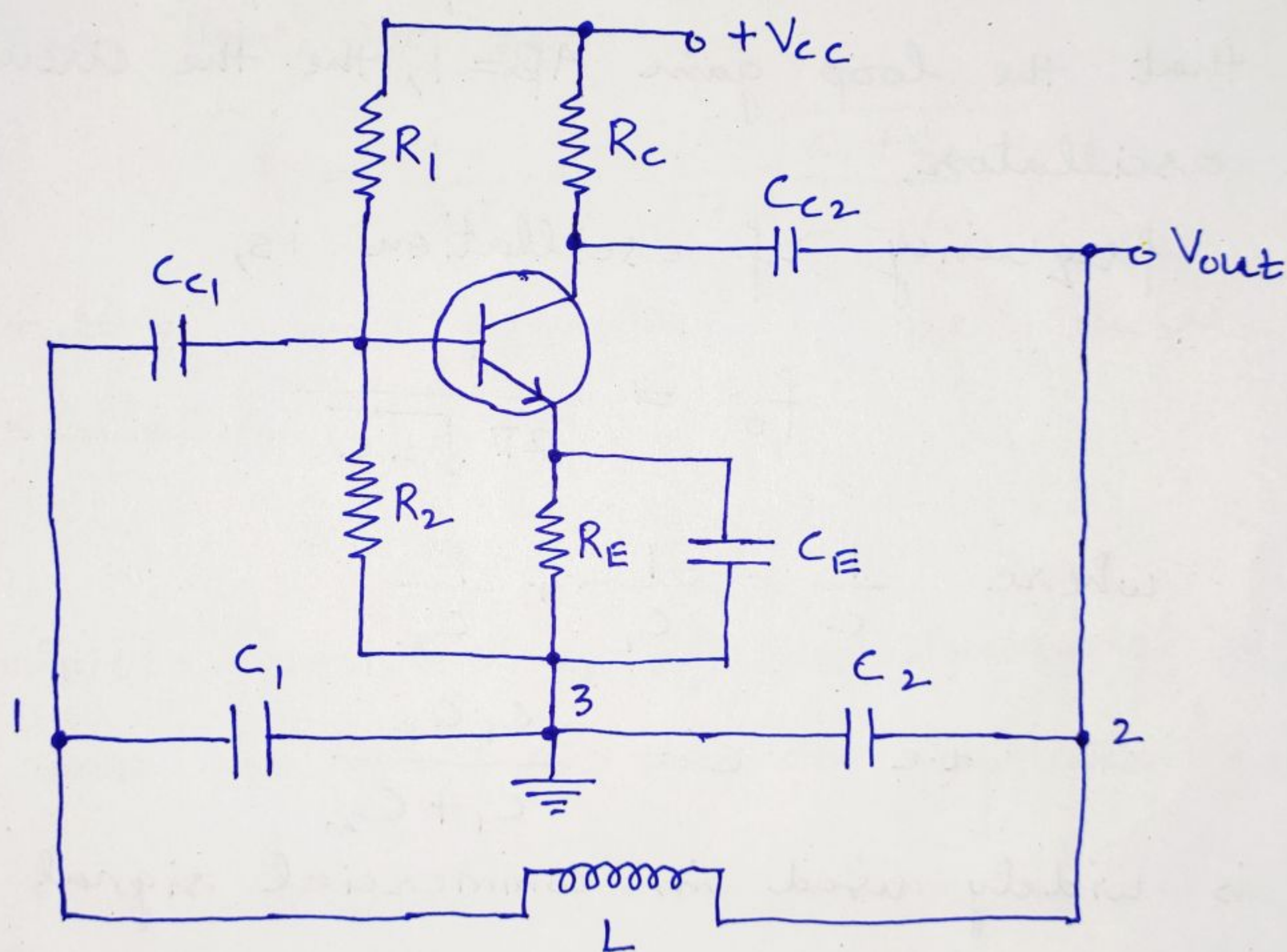


Figure 1. Colpitts Oscillator.

When the supply voltage  $+V_{cc}$  is switched ON, a transient current is produced in the tank circuit and consequently, damped oscillations are set up in the circuit. The oscillatory current in the tank circuit produces ac voltage across  $C_1$  and  $C_2$ . As terminal 3 is earthed, it will be at zero potential. If terminal 1 is at a positive potential with respect to 3 at



any instant, terminal 2 will be at a negative (2) potential with respect to 3 at the same instant. Thus, the phase difference between the terminals 1 and 2 is always  $180^\circ$ . In the CE mode, the transistor provides the phase difference of  $180^\circ$  between the input and output. Therefore, the total phase shift is  $360^\circ$ . Thus, at the frequency determined for the tank circuit, the necessary condition for sustained oscillations is satisfied. If the feedback is adjusted so that the loop gain  $A\beta = 1$ , then the circuit acts as an oscillator.

The frequency of oscillation is,

$$f_o = \frac{1}{2\pi \sqrt{LC}}$$

$$\text{where } \frac{1}{C} = \frac{1}{C_1} + \frac{1}{C_2}$$

$$\text{i.e. } C = \frac{C_1 C_2}{C_1 + C_2}$$

It is widely used in commercial signal generators for frequencies between 1 MHz and 500 MHz. It is also used as a local oscillator in superheterodyne radio receiver.

Analysis: For this oscillator

$$Z_1 = \frac{1}{j\omega C_1} = -\frac{j}{\omega C_1}$$

$$Z_2 = \frac{1}{j\omega C_2} = -\frac{j}{\omega C_2}$$



$$Z_3 = j\omega L$$

(3)

Substituting these values in the general equation of oscillators,

i.e. 
$$h_{ie}(Z_1 + Z_2 + Z_3) + Z_1 Z_2 (1 + h_{fe}) + Z_1 Z_3 = 0$$

$$\therefore -j h_{ie} \left( \frac{1}{\omega C_1} + \frac{1}{\omega C_2} - \omega L \right) + \left( \frac{1 + h_{fe}}{\omega^2 C_1 C_2} - \frac{L}{C_1} \right) = 0$$

The frequency of oscillation  $f_0 = \frac{\omega_0}{2\pi}$  is found by equating the imaginary part of above equation to zero. Thus, we get

$$f_0 = \frac{\omega_0}{2\pi} = \frac{1}{2\pi} \sqrt{\frac{C_1 + C_2}{L C_1 C_2}}$$

Substituting above equation in the general equation for oscillator,

$$h_{fe} = \frac{C_2}{C_1}$$

In Colpitts oscillator, if the loading effect of the base is ignored, then the feedback fraction becomes  $\beta = \frac{C_2}{C_1}$ . For oscillations to occur, the voltage gain  $A_v$  must be greater than  $\frac{1}{\beta}$ , i.e.

$$A_v > \frac{C_1}{C_2}$$

Q1. In the Hartley oscillator,  $L_1 = 0.4 \text{ mH}$  and  $C = 0.004 \text{ }\mu\text{F}$ . If the frequency of the oscillator is  $120 \text{ kHz}$ , find the value of  $L_2$ . Neglect the mutual inductance.

Solution: The frequency of Hartley oscillator is given by



$$f_0 = \frac{1}{2\pi \sqrt{(L_1 + L_2)C}}$$

Therefore, 
$$L_2 = \frac{1}{4\pi^2 f_0^2 C} - L_1$$

$$L_2 = \frac{1}{4\pi^2 (120 \times 10^3)^2 \times 0.004 \times 10^{-6}} - 0.4 \times 10^{-3}$$

$$L_2 = 0.44 \times 10^{-3} - 0.4 \times 10^{-3} = 0.04 \text{ mH.}$$

Q2. In the Colpitts oscillator,  $C_1 = 0.2 \mu\text{F}$  and  $C_2 = 0.02 \mu\text{F}$ . If the frequency of the oscillator is 10 KHz, find the value of the inductor. Also find the required gain for oscillation.

Solution: The frequency of the Colpitts oscillator is given by

$$f_0 = \frac{1}{2\pi} \sqrt{\frac{C_1 + C_2}{LC_1 C_2}}$$

Therefore, 
$$L = \frac{C_1 + C_2}{4\pi^2 f_0^2 C_1 C_2}$$

$$L = \frac{0.22 \times 10^{-6}}{4\pi^2 \times (10 \times 10^3)^2 \times 0.2 \times 10^{-6} \times 0.02 \times 10^{-6}}$$

$$L = 13.932 \text{ mH.}$$

The voltage gain required to produce oscillation is,

$$A_v > \frac{C_1}{C_2} = \frac{0.2 \times 10^{-6}}{0.02 \times 10^{-6}} = 10$$


---



Q.3. In a Hartley oscillator, the two inductances (5) are  $20 \mu\text{H}$  and  $2 \text{ mH}$  while the frequency is to be changed from  $950 \text{ KHz}$  to  $2050 \text{ KHz}$ . Calculate the range over which the capacitor is to be varied.

Solution: Given for a Hartley Oscillator,

$$L_1 = 20 \mu\text{H}$$

$$L_2 = 2 \text{ mH}$$

$$f_1 = 950 \text{ KHz}$$

$$f_2 = 2050 \text{ KHz}$$

Now, frequency of oscillations of the Hartley oscillator is

$$f_o = \frac{1}{2\pi \sqrt{(L_1 + L_2)C}}$$

$$\therefore C = \frac{1}{4\pi^2 (L_1 + L_2) f_o^2}$$

When  $f_o = 950 \text{ KHz}$ ,

$$C = \frac{1}{4\pi^2 [20 \times 10^{-6} + 2 \times 10^{-3}] (950 \times 10^3)^2} = 13.89 \text{ pF}$$

When  $f_o = 2050 \text{ KHz}$ ,

$$C = \frac{1}{4\pi^2 [20 \times 10^{-6} + 2 \times 10^{-3}] (2050 \times 10^3)^2} = 2.98 \text{ pF}$$

Hence, the range of capacitance is from  $2.98 \text{ pF}$  to  $13.89 \text{ pF}$ .

Q.4. A Colpitts oscillator is designed with  $C_1 = 7500 \text{ pF}$  and  $C_2 = 100 \text{ pF}$ . The inductance is variable. Determine the range of inductance values, if the frequency of



oscillation is to vary between 950 KHz and 2050 KHz. (6)

Solution: Given  $C_1 = 7500 \text{ pF}$ ,  $C_2 = 100 \text{ pF}$

$$\therefore C = \frac{C_1 C_2}{C_1 + C_2} = 98.68 \times 10^{-12} \text{ F}$$

Now, for Colpitts oscillator,

$$f_0 = \frac{1}{2\pi \sqrt{LC}}$$

$$\text{or, } L = \frac{1}{4\pi^2 \cdot C \cdot f_0^2}$$

When  $f_0 = 950 \text{ KHz}$ ,

$$L = \frac{1}{4\pi^2 [98.68 \times 10^{-12}] [950 \times 10^3]^2}$$

$$L = 284 \mu\text{H}$$

When  $f_0 = 2050 \text{ KHz}$ ,

$$L = \frac{1}{4\pi^2 [98.68 \times 10^{-12}] [2050 \times 10^3]^2}$$

$$L = 61 \mu\text{H}$$

Hence, the range of inductance required is from 61  $\mu\text{H}$  to 284  $\mu\text{H}$ .

---



Q1. Which of the following network is used to give feedback to transistor in Colpitts oscillator?

- (a) inductive fixed bias
- (b) capacitive fixed bias
- (c) inductive voltage divider
- (d) capacitive voltage divider

Q2. How many capacitors are there in the tank circuit of Colpitts oscillator?

- (a) 1
- (b) 2
- (c) 3
- (d) 0

Q3. How many inductors are there in the tank circuit of Colpitts oscillator?

- (a) 1
- (b) 2
- (c) 3
- (d) 0

Q4. Active element used in Colpitts oscillator is

- (a) cell
- (b) Voltage regulator
- (c) Diode
- (d) Transistor

Q5. Capacitive circuit configuration in Colpitts oscillator improves

- (a) Bulkiness
  - (b) Frequency stability
  - (c) Impedance
  - (d) Appearance
-